

Building a RISC-V Core in Makerchip with TL-Verilog



Steve Hoover

Founder, Redwood EDA

July 31, 2020




Agenda

- Digital logic design
 - Logic gates
 - Makerchip platform
 - Combinational logic
 - Sequential logic
 - Pipelined logic
 - State
- Simple RISC-V subset
- Pipelined RISC-V subset
- Complete (almost) RISC-V (RV32I)

Digital Logic

 The real world is analog... complicated... imperfect.




Analog

 nuanced, imperfect, subject to noise, lossy










Digital

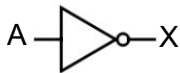well-defined, precise, resilient, reproducible



Logic Gates

Name	NOT	AND	OR	XOR	NAND	NOR	XNOR																																																																																																
Symbol																																																																																																							
Truth Table	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
A	B	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
A	B	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
A	B	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
A	B	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
A	B	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
A	B	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					




Implementing Digital Logic

Digital logic can be implemented using:

- Semiconductors/transistors
- Mechanics
- Vacuum tubes
- Fluidics
- Optics
- Quantum properties
- DNA
- etc.


This course is not specific to any particular implementation technology, though supplemental material may target ASIC or FPGA flows.

Combinational Circuit

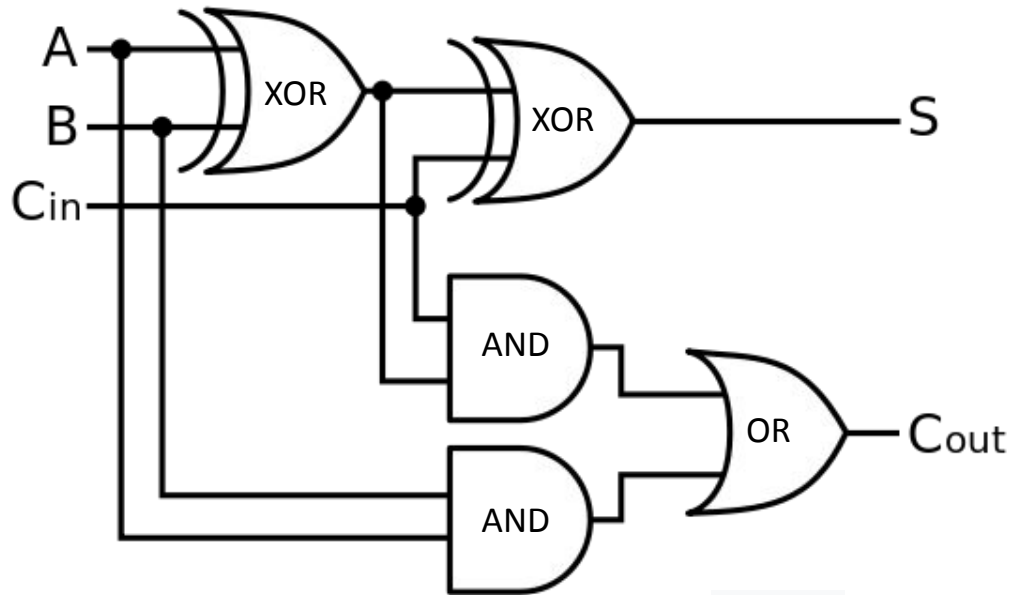

[CC BY-SA 3.0](#)
[en:User:Cburnett](#)


Combinational Circuit

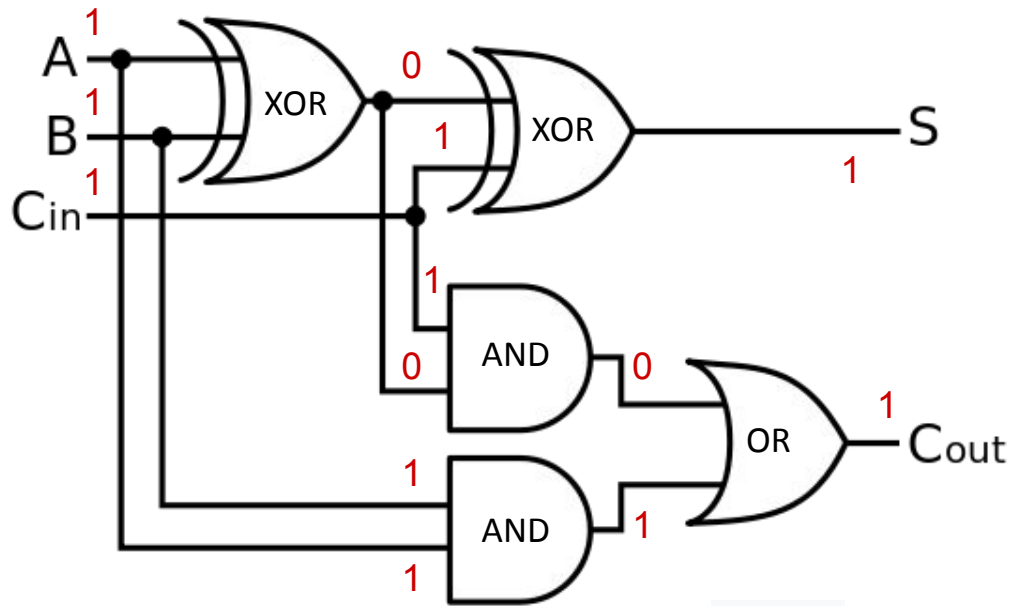

[CC BY-SA 3.0](#)
[en:User:Cburnett](#)

Adder




 



$$S = A + B$$

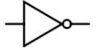


Adder



Boolean Operators


Op	Bool Arith	Bool Calc	Verilog	Gate
NOT	\overline{A}	$\neg A$	$\sim A$ (or $!A$)	
AND	$A \bullet B$	$A \wedge B$	$A \& B$ (or $\&\&$)	
OR	$A + B$	$A \vee B$	$A B$ (or $ $)	
XOR	$A \oplus B$	$A \oplus B$	$A \wedge B$	
NAND	$\overline{A \bullet B}$	$\neg (A \wedge B)$	$! (A \& B)$	
NOR	$\overline{A + B}$	$\neg (A \vee B)$	$! (A B)$	
XNOR	$\overline{A \oplus B}$	$\neg (A \oplus B)$	$! (A \wedge B)$	

Multiplexer (MUX)


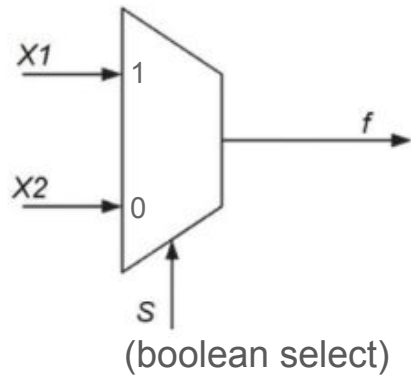


Verilog:

```
assign f = s ? X1 : X2;
```

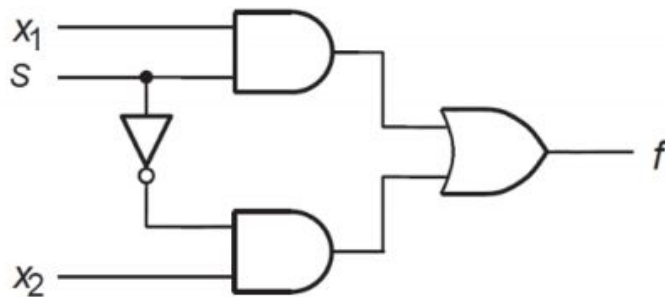

Chaining Ternary Operator

 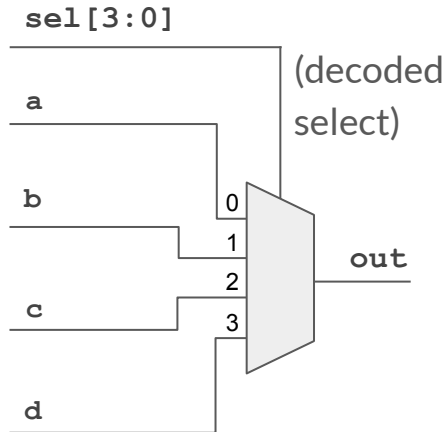

Verilog:

```
assign f =  
    sel[3]  
        ? d  
        : (sel[2]  
            ? c  
            : (sel[1]  
                ? b  
                : a  
            )  
        );
```

Equivalently:

```
assign f =  
    sel[3]  
        ? d :  
    sel[2]  
        ? c :  
    sel[1]  
        ? b :  
    //default  
    a;
```

(So, highest
priority first.)

Makerchip

makerchip PROJECT TUTORIALS HELP saved 4 minutes ago

EDITOR NAV-TLV LOG

```
@1
Saa_sq[7:0] = $aa[3:0] ** 2;
Sbb_sq[7:0] = $bb[3:0] ** 2;
@2
Scc_sq[8:0] = Saa_sq + Sbb_sq;
@3
Scc[4:0] = sqrt(Scc_sq);
```

Last updated 10 minutes ago

TUTORIAL-VALID x

|calc

Figure 1: Pipelined Pythagorean Theorem Logic

This pipeline is 3 cycles deep. It has a throughput of one transaction per cycle, where a transaction performs one Pythagorean Theorem calculation per cycle.

DIAGRAM

Last updated 10 minutes ago


WAVEFORM

ZOOM IN ZOOM OUT ZOOM FULL << >>

Signal	Value
clk	1
TLV	1
calc	1

Last updated 10 minutes ago


Lab: Makerchip Platform

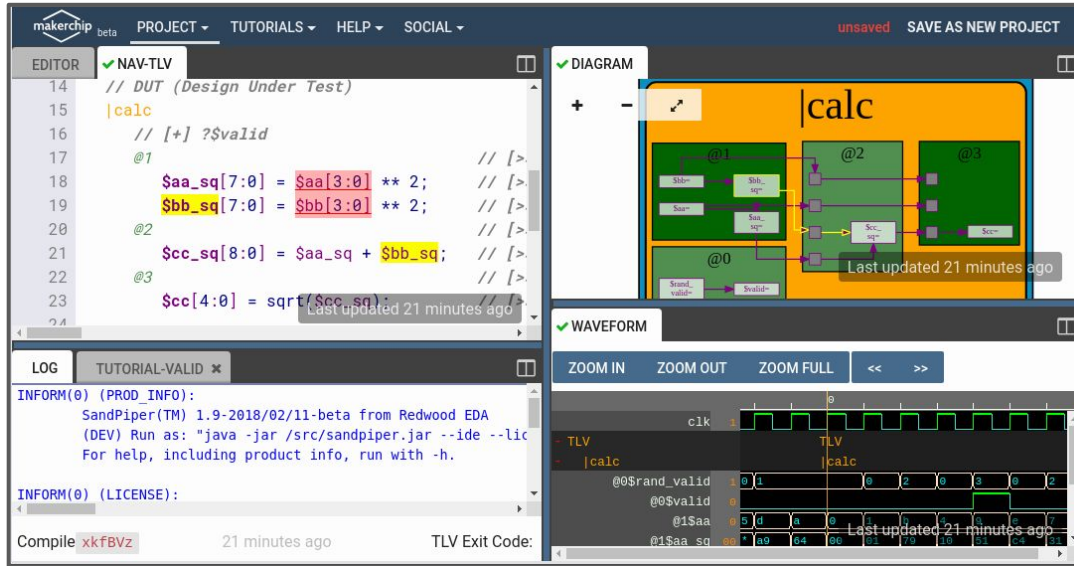

Reproduce this screenshot:

1. Open “Tutorials” “Validity Tutorial”.
2. In tutorial, click

Load Pythagorean Example

3. Split panes  and move tabs.
4. Zoom/pan in Diagram w/ mouse wheel and drag.
5. Zoom Waveform w/ “Zoom In” button.
6. Click `$bb_sq` to highlight.

1. On desktop machine, in modern web browser (not IE), go to: makerchip.com
2. Click “Launch Makerchip IDE”.

Lab: Combinational Logic

A) Inverter

1. Open “Examples” (under “Learn”).
2. Load “Makerchip Default Template” (under “Bare-Bones Templates”).
3. Make an inverter.

On line 16, in place of:

```
//...
```

type:

```
$out = ! $in1;
```

(Preserve 3-space indentation, no tabs)

4. Compile (“E” menu) & Explore

Note:

There was no need to declare `$out` and `$in1` (unlike Verilog).

There was no need to assign `$in1`. Random stimulus is provided, and a warning is produced.

B) Other logic

Make a 2-input gate.

(Boolean operators: (&&, ||, ^))



Lab: Vectors

`$out[4:0]` creates a “vector” of 5 bits.

Arithmetic operators operate on vectors as binary numbers.


1. Try:

```
$out[4:0] = $in1[3:0] + $in2[3:0];
```

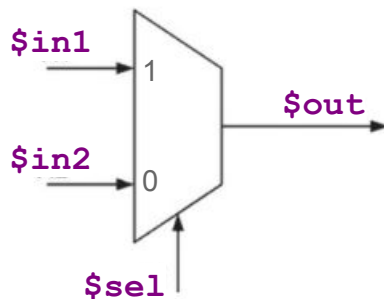
2. View Waveform.

Lab: Mux

`$out = $sel ? $in1 : $in2;`
creates a multiplexer.



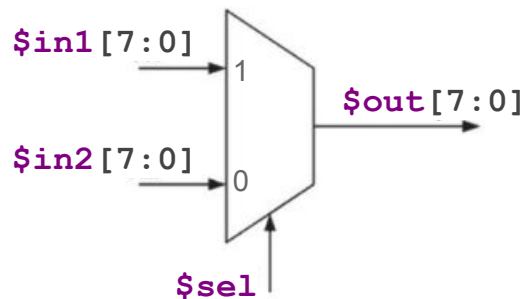Modify this multiplexer to operate on vectors.




Note that bit ranges can generally be assumed on the right-hand side, but with no assignments to these signals, they must be explicit.

Lab: Combinational Calculator

This circuit implements a calculator that can perform +, -, *, / on two input values.

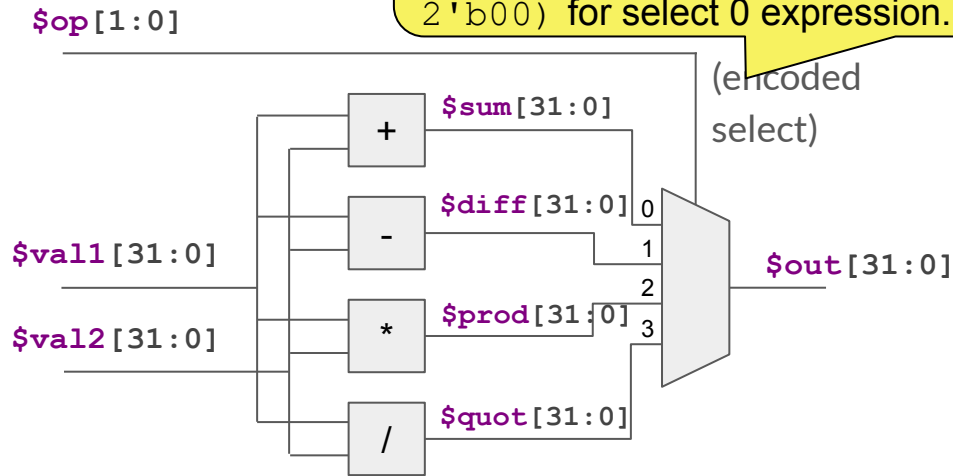Oops! Syntax for these MUX selects was not yet introduced.
Use e.g. (`$op[1:0] == 2'b00`) for select 0 expression.



1. Implement this.

2. Use:

```
$val1[31:0] = $rand1[31:0];  
$val2[31:0] = $rand2[31:0];
```

for inputs to keep values small.

3. We'll return to this, so "Save as new project", bookmark, and open a new Makerchip IDE in a new tab.

Sequential Logic

Sequential logic is sequenced by a clock signal.



A D-flip-flop transitions next state to current state on a rising clock edge.




The circuit is constructed to enter a known state in response to a reset signal.




Sequential Logic

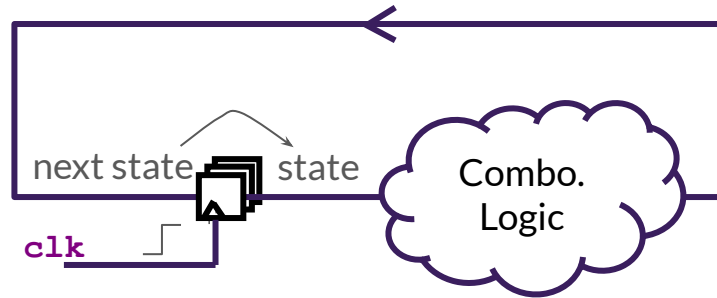The whole circuit can be viewed as a big state machine.




Sequential Logic - Fibonacci Series

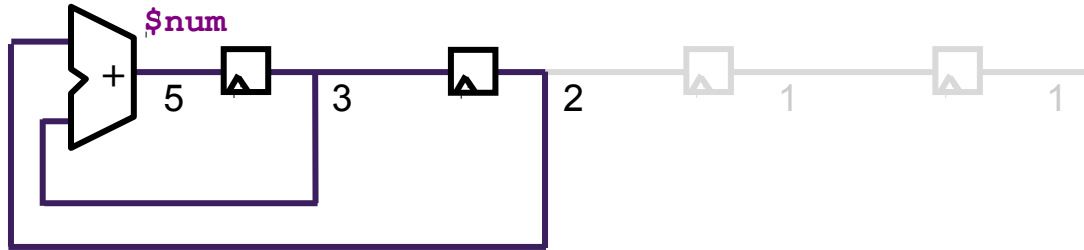Next value is sum of previous two: 1, 1, 2, 3, 5, 8, 13, ...



Fibonacci Series - Reset

 
Next value is sum of previous two: 1, 1, 2, 3, 5, 8, 13, ...



```
$num[31:0] = $reset ? 1 : (>>1$num + >>2$num);
```


Lab: Counter

1. Design a free-running counter:

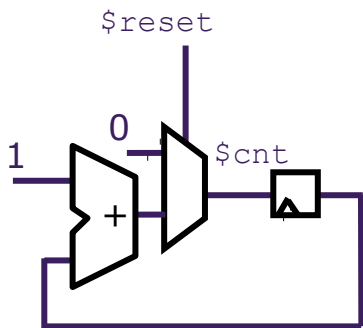

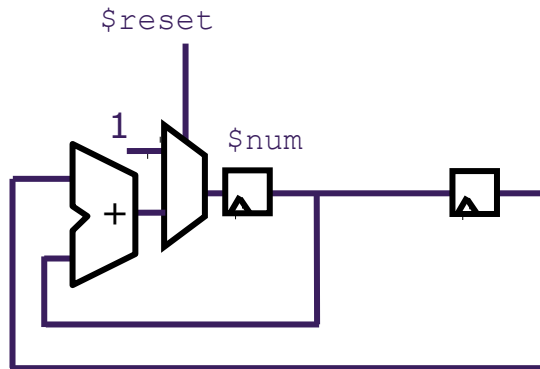2. Include this code in your saved calculator sandbox for later (and confirm that it auto-saves).

Reference Example: Fibonacci Sequence (1, 1, 2, 3, 5, 8, ...)



```
\TLV
  $num[31:0] = $reset ? 1 : (>>1$num + >>2$num);
```

3-space indentation
(no tabs)

Values in Verilog

16 ' h F0

16-bit hexadecimal value

' 0: All 0s (width based on context).

' X: All DONT-CARE bits.

16 ' d5: 16-bit decimal 5.

5 ' b00XX1: 5-bit value with DONT-CARE bits.

1: 32-bit (signed) 1.


Our simulator configuration:

- will zero-extend or truncate when widths are mismatched (without warning)
- uses 2-state simulation (no X's)

Lab: Sequential Calculator


A real calculator remembers the last result, and uses it for the next calculation.

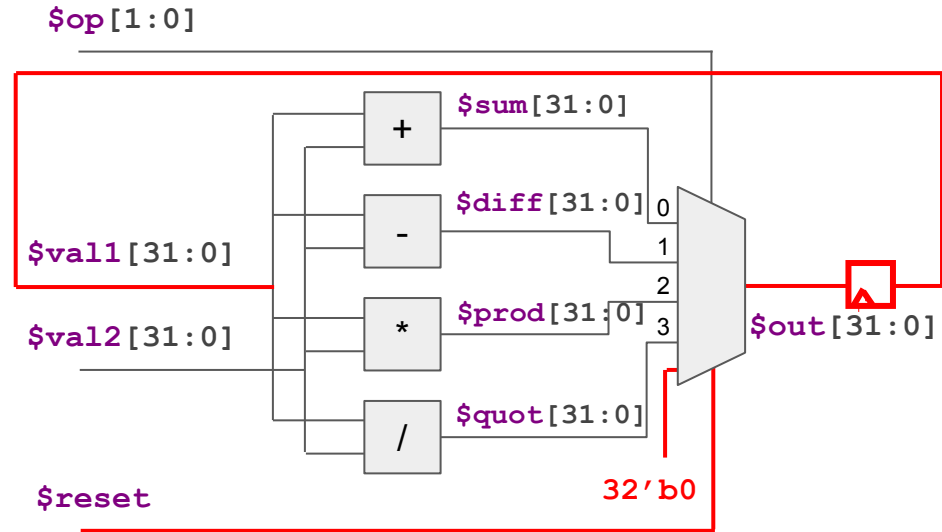1. Return to the calculator.
2. Update the calculator to perform a new calculation each cycle where
 $\$val1[31:0]$ = the result of the previous calculation.
3. Reset $\$out$ to zero.
4. Copy code and save outside of Makerchip (just to be safe).




A Simple Pipeline

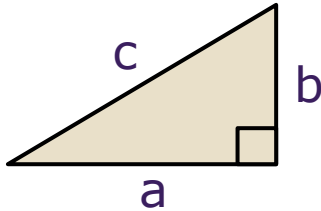
Let's compute Pythagoras's Theorem in hardware.



$$c = \text{sqrt}(a^2 + b^2)$$

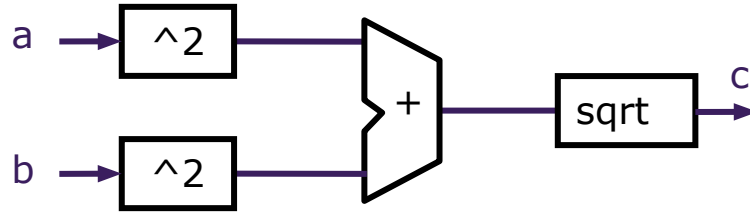


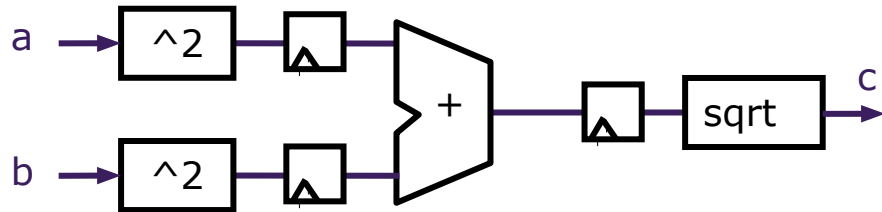We distribute the calculation over three cycles.




A Simple Pipeline - Timing-Abstract

RTL:

 


Timing-abstract:

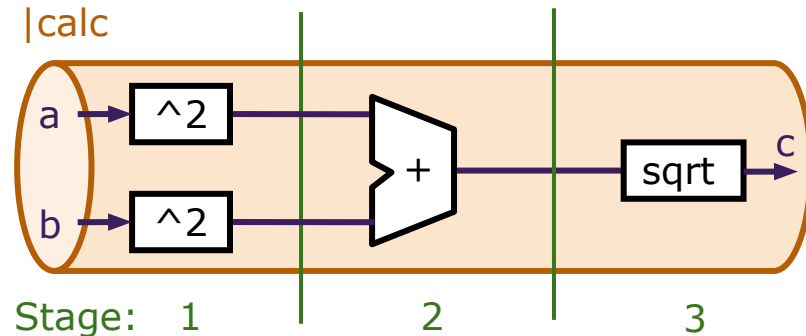

→ Flip-flops and staged signals are implied from context.


A Simple Pipeline - TL-Verilog

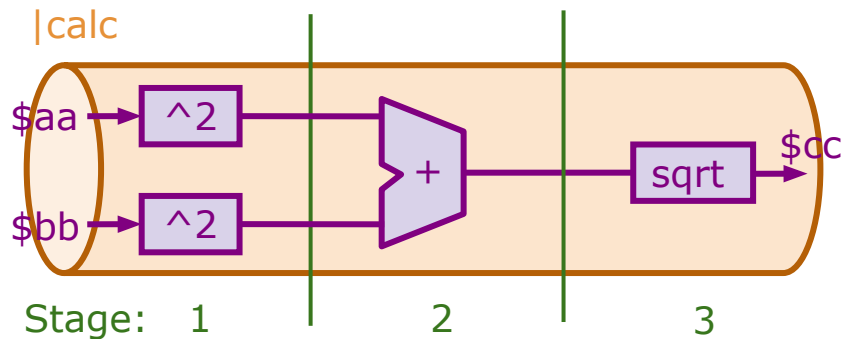

TL-Verilog

```
|calc
@1
    $aa_sq[31:0] = $aa * $aa;
    $bb_sq[31:0] = $bb * $bb;
@2
    $cc_sq[31:0] = $aa_sq + $bb_sq;
@3
    $cc[31:0] = sqrt($cc_sq);
```

SystemVerilog vs. TL-Verilog

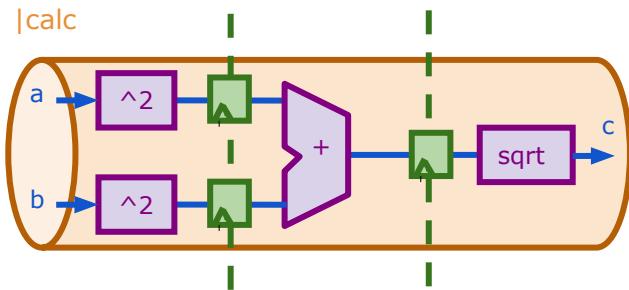

System
Verilog

~3.5x

TL-Verilog

```
|calc
@1
    $aa_sq[31:0] = $aa * $aa;
    $bb_sq[31:0] = $bb * $bb;
@2
    $cc_sq[31:0] = $aa_sq + $bb_sq;
@3
    $cc[31:0] = sqrt($cc_sq);
```

```
// Calc Pipeline
logic [31:0] a_C1;
logic [31:0] b_C1;
logic [31:0] a_sq_C1,
             a_sq_C2;
logic [31:0] b_sq_C1,
             b_sq_C2;
logic [31:0] c_sq_C2,
             c_sq_C3;
logic [31:0] c_C3;
always_ff @(posedge clk) a_sq_C2 <= a_sq_C1;
always_ff @(posedge clk) b_sq_C2 <= b_sq_C1;
always_ff @(posedge clk) c_sq_C3 <= c_sq_C2;
// Stage 1
assign a_sq_C1 = a_C1 * a_C1;
assign b_sq_C1 = b_C1 * b_C1;
// Stage 2
assign c_sq_C2 = a_sq_C2 + b_sq_C2;
// Stage 3
assign c_C3 = sqrt(c_sq_C3);
```

Retiming -- Easy and Safe

|calc

@1

\$aa_sq[31:0] = \$aa * \$aa;

\$bb_sq[31:0] = \$bb * \$bb;

@2

\$cc_sq[31:0] = \$aa_sq + \$bb_sq;

@3

\$cc[31:0] = sqrt(\$cc_sq);

|calc

@0

\$aa_sq[31:0] = \$aa * \$aa;

@1

\$bb_sq[31:0] = \$bb * \$bb;


@2

\$cc_sq[31:0] = \$aa_sq + \$bb_sq;

@4


\$cc[31:0] = sqrt(\$cc_sq);

|calc

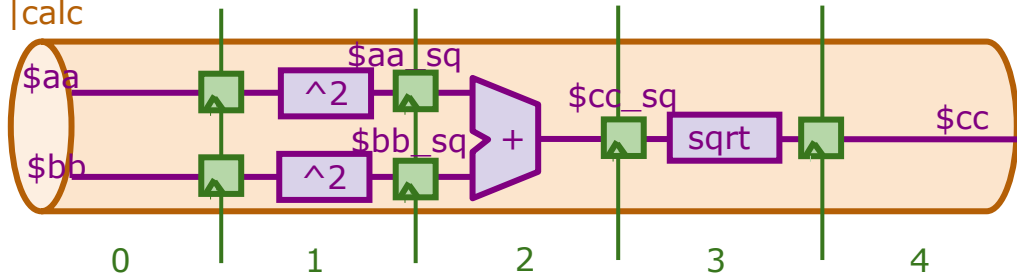

==

|calc

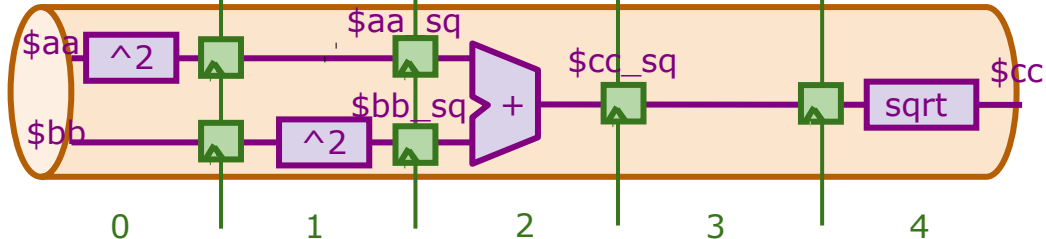



Staging is a physical attribute. No impact to behavior.

Retiming in SystemVerilog

```
// Calc Pipeline
logic [31:0] a_C1;
logic [31:0] b_C1;
logic [31:0] a_sq_C0,
           a_sq_C1,
           a_sq_C2;
logic [31:0] b_sq_C1,
           b_sq_C2;
logic [31:0] c_sq_C2,
           c_sq_C3,
           c_sq_C4;
logic [31:0] c_C3;
always_ff @(posedge clk) a_sq_C2 <= a_sq_C1;
always_ff @(posedge clk) b_sq_C2 <= b_sq_C1;
always_ff @(posedge clk) c_sq_C3 <= c_sq_C2;
always_ff @(posedge clk) c_sq_C4 <= c_sq_C3;
// Stage 1
assign a_sq_C1 = a_C1 * a_C1;
assign b_sq_C1 = b_C1 * b_C1;
// Stage 2
assign c_sq_C2 = a_sq_C2 + b_sq_C2;
// Stage 3
assign c_C3 = sqrt(c_sq_C3);
```

VERY BUG-PRONE!

High Frequency

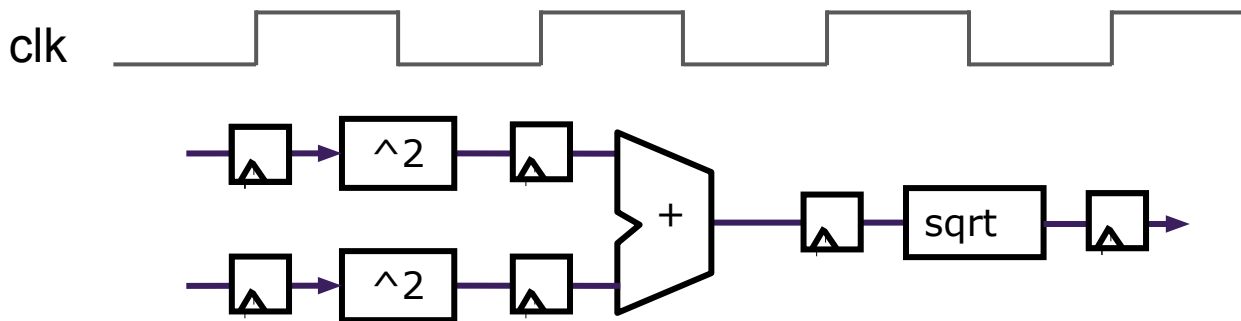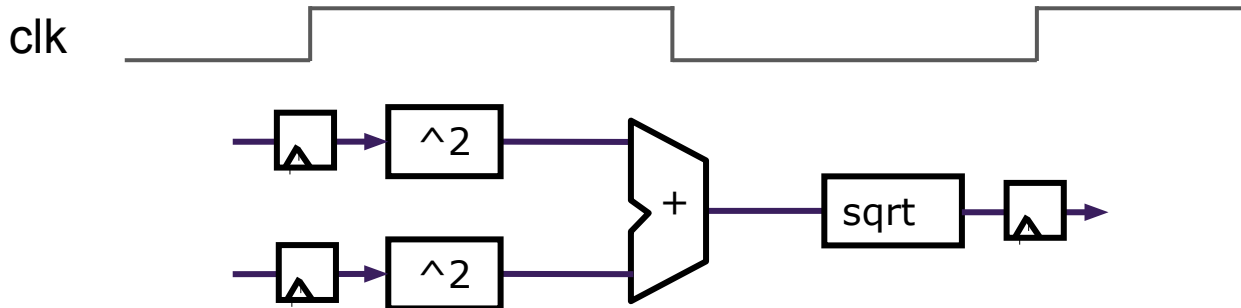




Makerchip - a level deeper

(Exploration of pipelined logic within Makerchip.)

Identifiers and Types

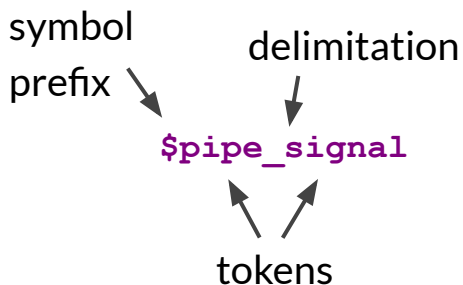Type of an identifier determined by symbol prefix and case/delimitation style. E.g.:



First token must start with two alpha chars. These determine delimitation style

- `$lower_case`: pipe signal
- `$CamelCase`: state signal (technically, this is "Pascal case")
- `$UPPER_CASE`: keyword signal

Numbers end tokens (after alphas)

- `$base64_value`: good
- `$bad_name_5`: bad


Numeric identifiers

- `>>1`: ahead by 1



Lab: Pipeline

See if you can produce this:

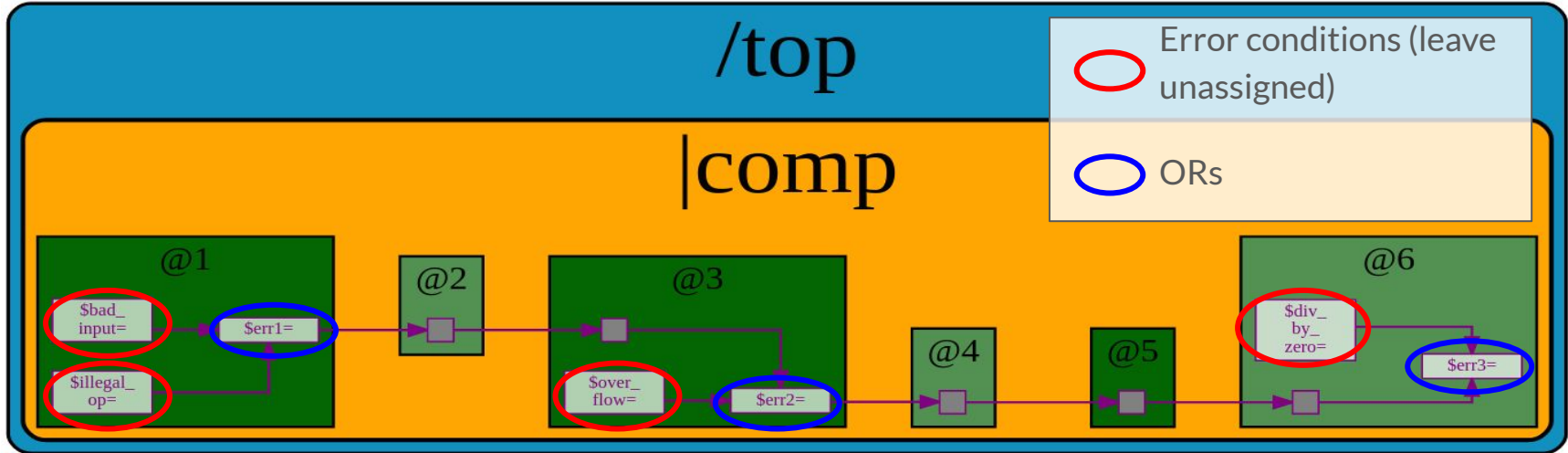

which ORs together (|) various error conditions that can occur within a computation pipeline.


[Open Solution in Makerchip](#)

(Ctrl-Click for new tab)

Lab: Counter and Calculator in Pipeline

1. Put calculator and counter in stage @1 of a |calc pipeline.
2. Check log, diagram, and waveform.
3. Confirm save.

 The `$reset = *reset` expression should be moved under the pipeline and pipestage as well.





What to do when you are stuck

When your stuck, and human help is not available:

- Always check the LOG, and resolve unexpected warnings/errors.
- Review previous lectures.
- Check any available supplemental material, chat forums, etc. accompanying the workshop.
- Check your understanding by comparing with the reference solution.
(Relying too heavily on this will slow you down. Understand before moving forward.)



Lab: Calculator Template Code with VIZ


Update your calculator to use the starting-point template, using, for example, the following steps:

1. Find the calculator starting-point template provided with this workshop, and open it in a new Makerchip session.
2. Paste your calculator logic into this template as appropriate.
3. Compile, debug.
4. Uncomment the "cal_viz" macro instantiation.
5. Compile, debug, and explore VIZ.
6. Close the old session and save the new one.

Lab: 2-Cycle Calculator

At high frequency, we might need to calculate every other cycle.

 1. Change alignment of `$out` (to calculate every other cycle).
2. Change counter to single-bit (to indicate every other cycle).
3. Connect `$valid` (to clear alternate outputs).
4. Retime mux to @2 (to ease timing; no functional change).
5. Verify behavior in waveform.
6. Save.




Validity


```
|calc
@1
    $valid = ...;
    ?$valid
@1
    $aa_sq[31:0] = $aa * $aa;
    $bb_sq[31:0] = $bb * $bb;
@2
    $cc_sq[31:0] = $aa_sq + $bb_sq;
@3
    $cc[31:0] = sqr
```

Validity provides:

 - Easier debug
- Cleaner design
- Better error checking
- Automated clock gating





Clock Gating

 

- Motivation:
 - Clock signals are distributed to EVERY flip-flop.
 - Clocks toggle twice per cycle.
 - This consumes power.
- Clock gating avoids toggling clock signals.
- TL-Verilog can produce fine-grained gating (or enables).

Total Distance (Makerchip walkthrough)

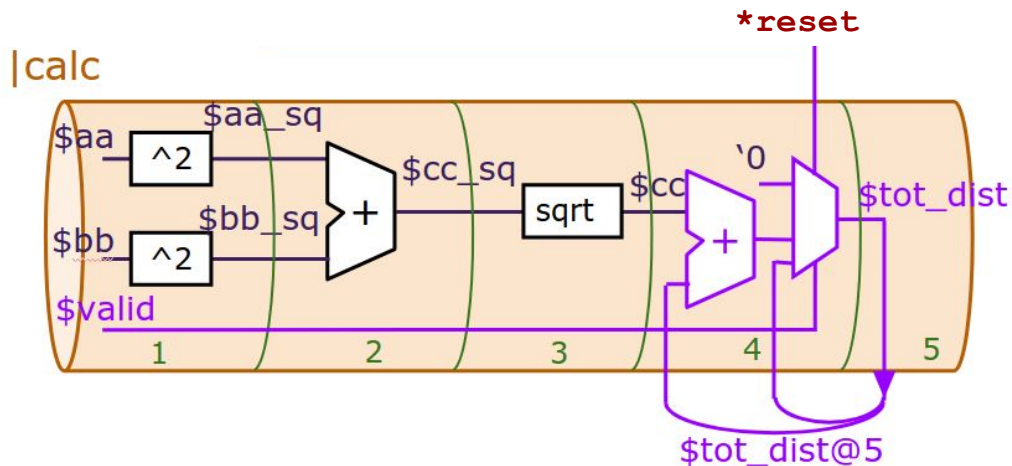 


Lab: 2-Cycle Calculator with Validity

1. Use:
 $\$valid_or_reset = \$valid \mid \$reset;$
as a when condition for calculation
instead of zeroing $\$out$.

For reference:

```
|calc
@1
  $valid = ...;
  ?? $valid
@1
  $aa_sq[31:0] = $aa * $aa;
  ...
```

2. Verify behavior in waveform.

 


Lab: Calculator with Single-Value Memory


Calculators support “mem” and “recall”, to remember and recall a value.

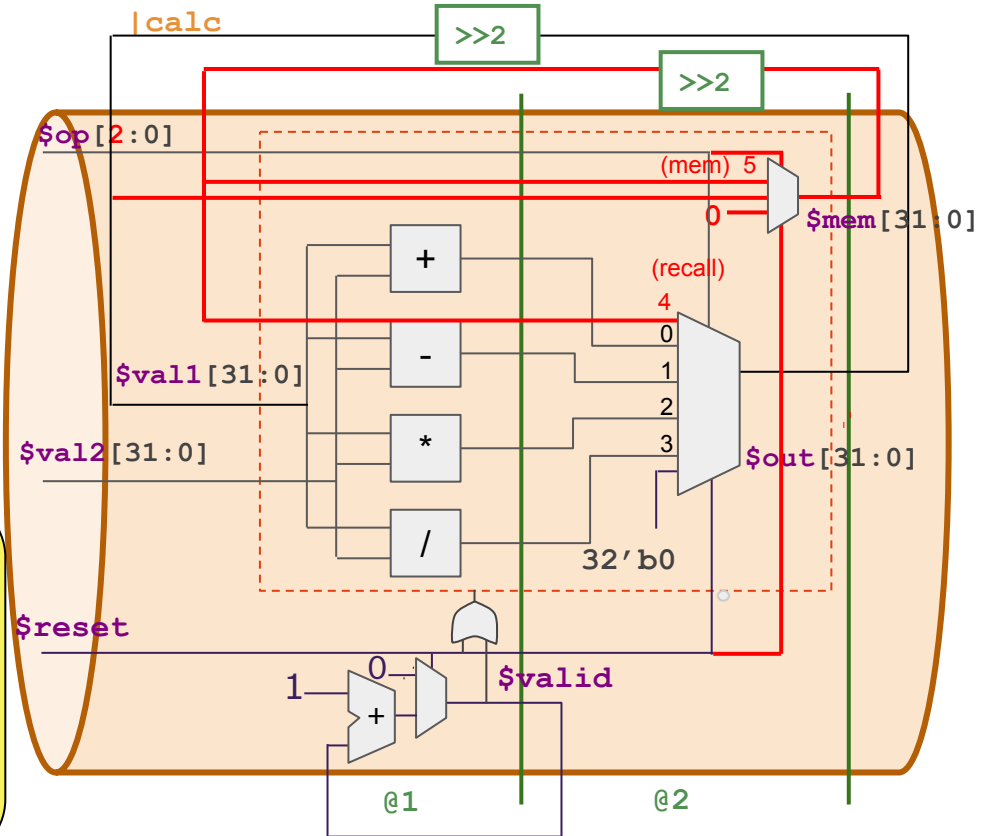1. Extend $\$op$ to 3 bits.
2. Add memory MUX.
3. Select recall value in output MUX.
4. Verify behavior in waveform.


Missing from this logic: it is necessary to provide a default recirculation of \$out for \$out mux. Previously there was no need for a "retain value" case, but now mem operations must retain \$out (and it doesn't hurt to retain for illegal (6, 7) op inputs as well).



Example RISC-V Block Diagram

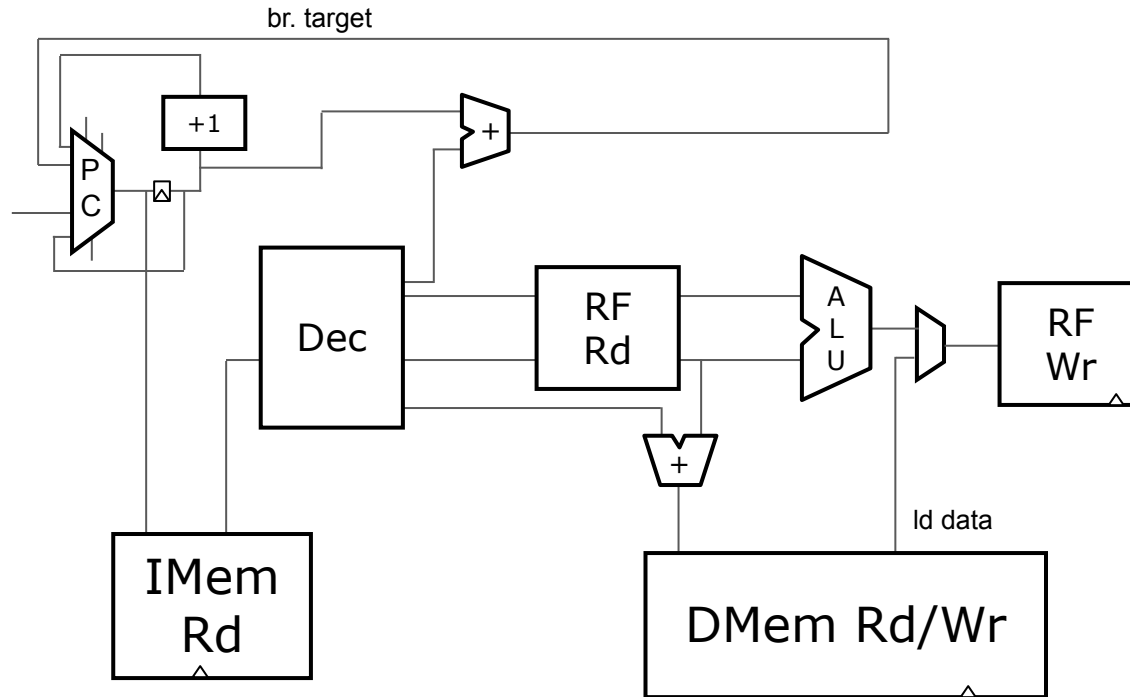


Implementation Plan

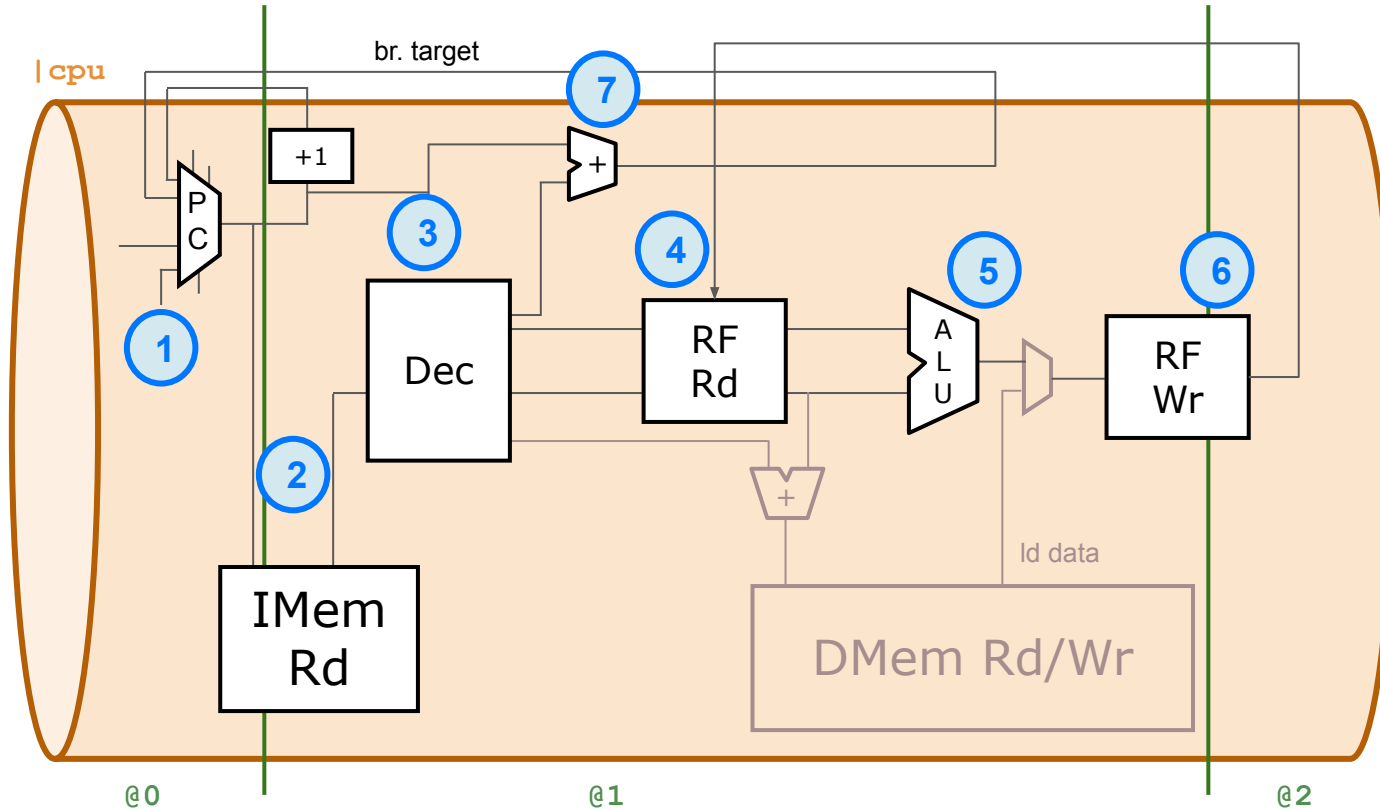

Lab: Next PC

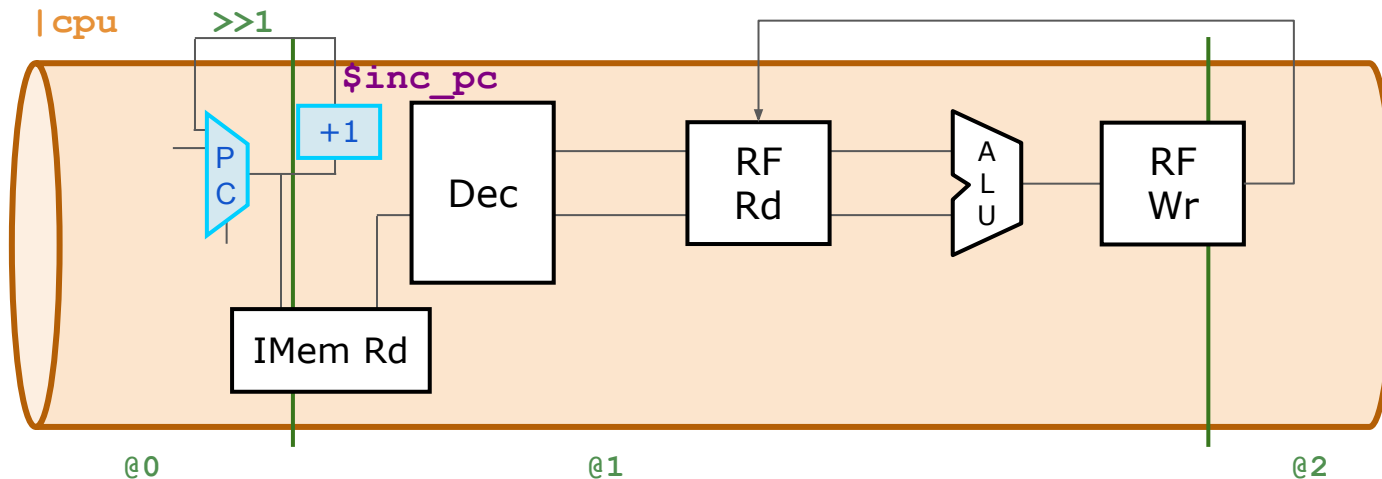
Reset $\$pc[31:0]$ to 0 if previous instruction was a “reset instruction” ($\gg 1 \$reset$), and increment by 1 instruction (32' 4 bytes) thereafter. (We'll add branch support later.)



Check PC value in simulation and confirm save. PC's after reset should be 0, 4, ...


Lab: Fetch (part 1)

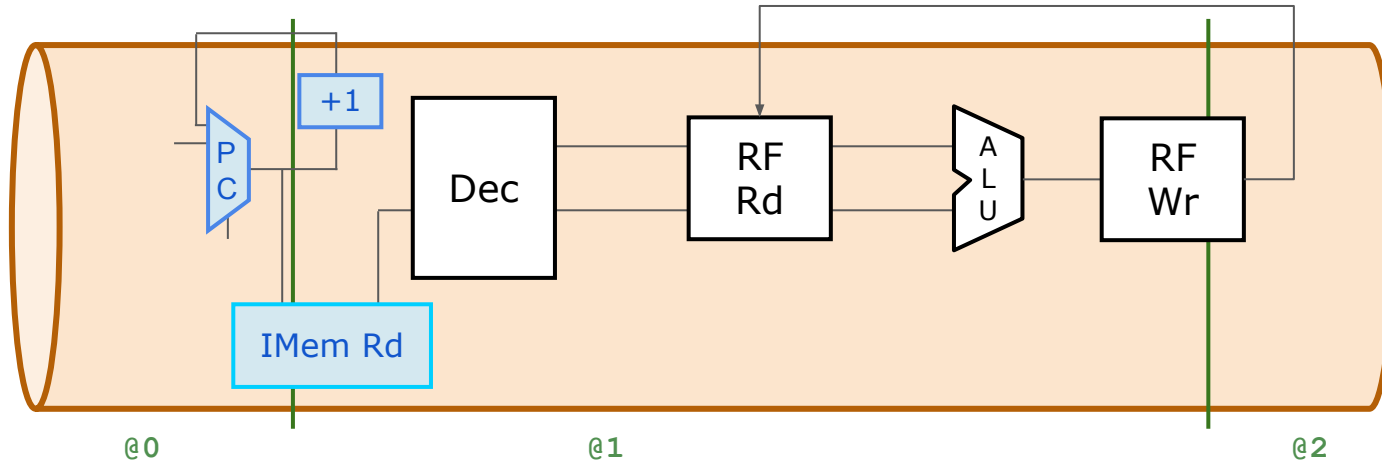Add the instruction memory containing the program (provided).




1. Uncomment `//m4+imem(@1)` compile, and observe LOG warnings.
2. Uncomment `//m4+cpu_viz(@4)` compile, and explore VIZ tab.

Lab: Fetch (part 2)

 

1. `imem` expects inputs:
 - a. In: `$imem_rd_en` (read enable)
 - b. In: `$imem_rd_addr`
`[M4_IMEM_INDEX_CNT-1:0]`
and provides output:
 - c. Out: `$imem_rd_data[31:0]`
2. Connect `imem` interface to read into `$instr[31:0]` addressed by `$pc[M4_IMEM_INDEX_CNT+1:2]` enabled every cycle after reset.
3. Check `$instr` in simulation and confirm save.

Decode

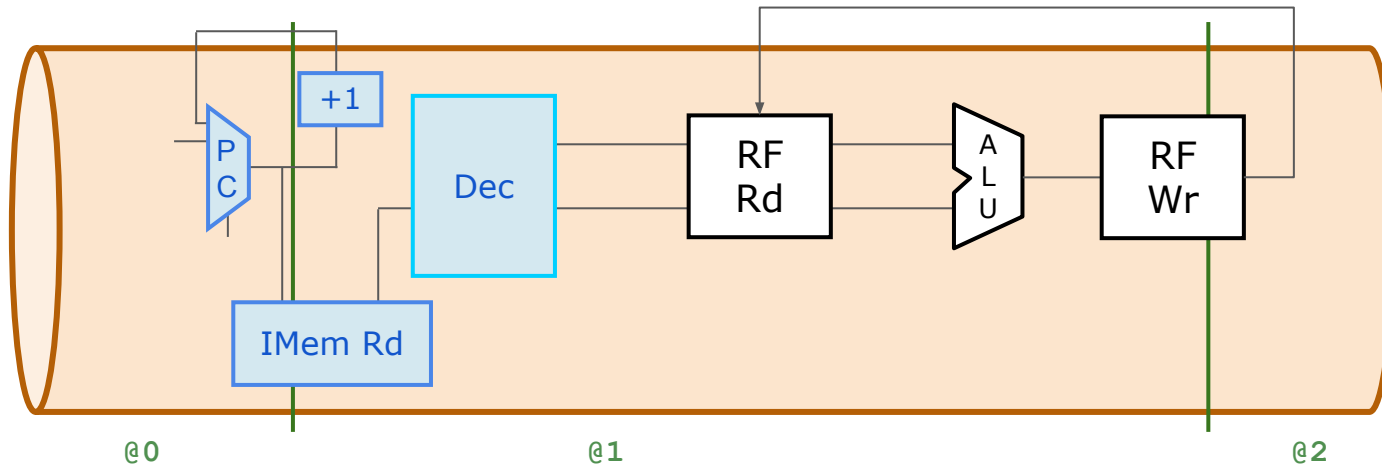

Lab: Instruction Types Decode

instr[6:2] determine instruction type: I, R, S, B, J, U

instr[4:2] instr[6:5]	000	001	010	011	100	101	110	111
00	I	I	-	-	I	U	I	-
01	S	S	-	R	R	U	R	-
10	R4	R4	R4	R4	R	-	-	-
11	B	I	-	J	I (unused)	-	-	-

```
$is_i_instr = $instr[6:2] ==? 5'b0000x ||  
              $instr[6:2] ==? 5'b001x0 ||  
              ...;  
...
```

Check behavior in simulation.

Lab: Instruction Immediate Decode

Form `$imm[31:0]` based on instruction type.


31	30	20	19	12	11	10	5	4	1	0	
— inst[31] —						inst[30:25]	inst[24:21]	inst[20]	I-immediate		
— inst[31] —						inst[30:25]	inst[11:8]	inst[7]	S-immediate		
— inst[31] —					inst[7]	inst[30:25]	inst[11:8]	0	B-immediate		
inst[31]	inst[30:20]		inst[19:12]		— 0 —						U-immediate
— inst[31] —			inst[19:12]		inst[20]	inst[30:25]	inst[24:21]	0	J-immediate		

```
$imm[31:0] = $is_i_instr ? { {21{$instr[31]}}, $instr[30:20] } :  
               $is_s_instr ? {...} :  
               ...;
```

Check behavior in simulation.

Lab: Instruction Decode

 Extract other instruction fields: `$funct7`, `$funct3`, `$rs1`, `$rs2`, `$rd`, `$opcode`




```
$rs2[4:0] = $instr[24:20];  
...
```

Check behavior in simulation.

Lab: RISC-V Instruction Field Decode

Let's use when conditions

 

```
$rs2_valid = $is_r_instr || $is_s_instr || $is_b_instr;  
?$rs2_valid  
    $rs2[4:0] = $instr[24:20];  
...
```

Check behavior in simulation.

Lab: Instruction Decode

RV32I Base Instruction Set (except CSR*, FENCE, ECALL, EBREAK):

\$funct7 is not valid for SLLI/SRLI/SRAI, so we shouldn't be using it for these instructions. In any case, it will not actually cause any harm for this workshop.

opcode	funct3	Instruction
01101111		LUI
00101111		AUIPC
11011111		JAL
11001111		JALR
11000111	000	BEQ
11000111	001	BNE
11000111	100	BLT
11000111	101	BGE
11000111	110	BLTU
11000111	111	BGEU
00000111	000	LB
00000111	001	LH
00000111	010	LW
00000111	100	LBU
00000111	101	LHU
01000111	000	SB
01000111	001	SH
01000111	010	SW
00100111	000	ADDI
00100111	010	SLTI

funct7[5]	funct3	opcode	Instruction
	011	00100111	SLTIU
	100	00100111	XORI
	110	00100111	ORI
	111	00100111	ANDI
	001	00100111	SLLI
	101	00100111	SRLI
	101	00100111	SRAI
0	000	01100111	ADD
1	000	01100111	SUB
0	001	01100111	SLL
0	010	01100111	SLT
0	011	01100111	SLTU
0	100	01100111	XOR
0	101	01100111	SRL
1	101	01100111	SRA
0	110	01100111	OR
0	111	01100111	AND

Complete circled instructions.

```
$dec_bits[10:0] =
    {$funct7[5], $funct3, $opcode};
$is_beq = $dec_bits ==?
    11'bx_000_1100011;
```

```
// Until instrs are implemented,
// quiet down the warnings.
`BOGUS_USE($is_beq $is_bne ...)
```


backtick

(no comma)

Check behavior in simulation
and confirm save.

Actually, m4+viz also quiets these warnings, so not needed.


Register File Read

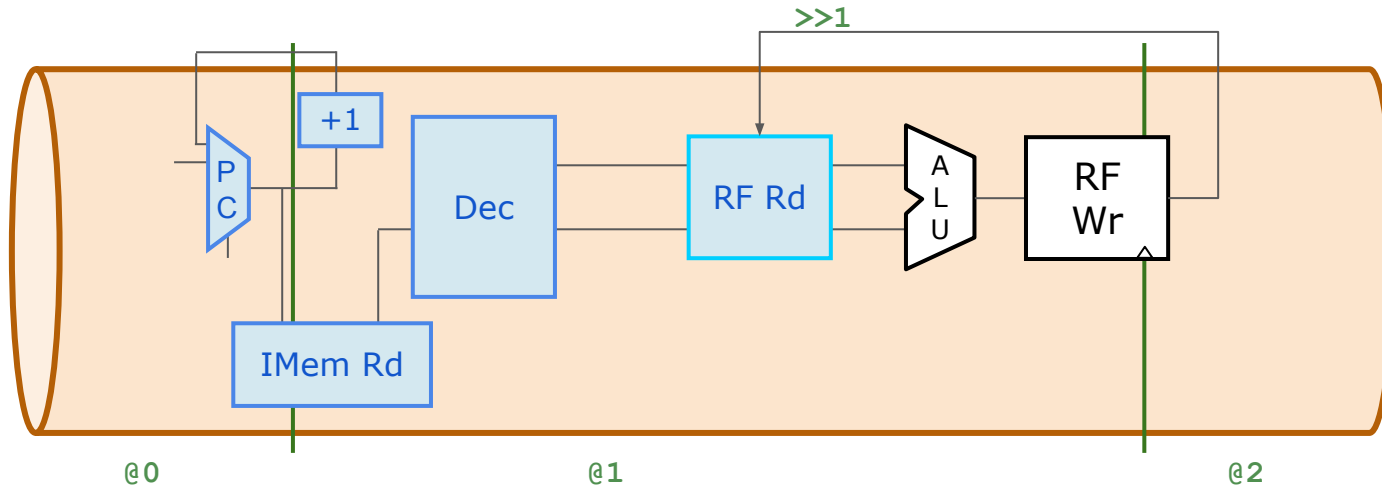


Lab: Register File Read

1. Uncomment `//m4+rf (@1,`
`@1)` instantiation, defining a
reg. file that reads and writes
at stage `@1`. (Dangling inputs
have default values.)
2. Provide proper input
assignments to enable RF read
(`rd`) of `$rs1/2` when
`$rs1/2_valid`.
3. Debug in simulation.

2-read, 1-write register file:

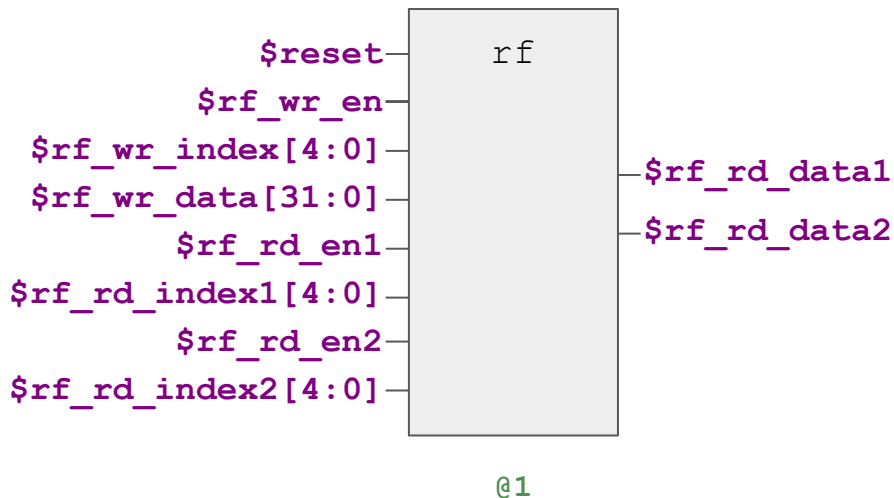


Lab: Register File Read (part 2)

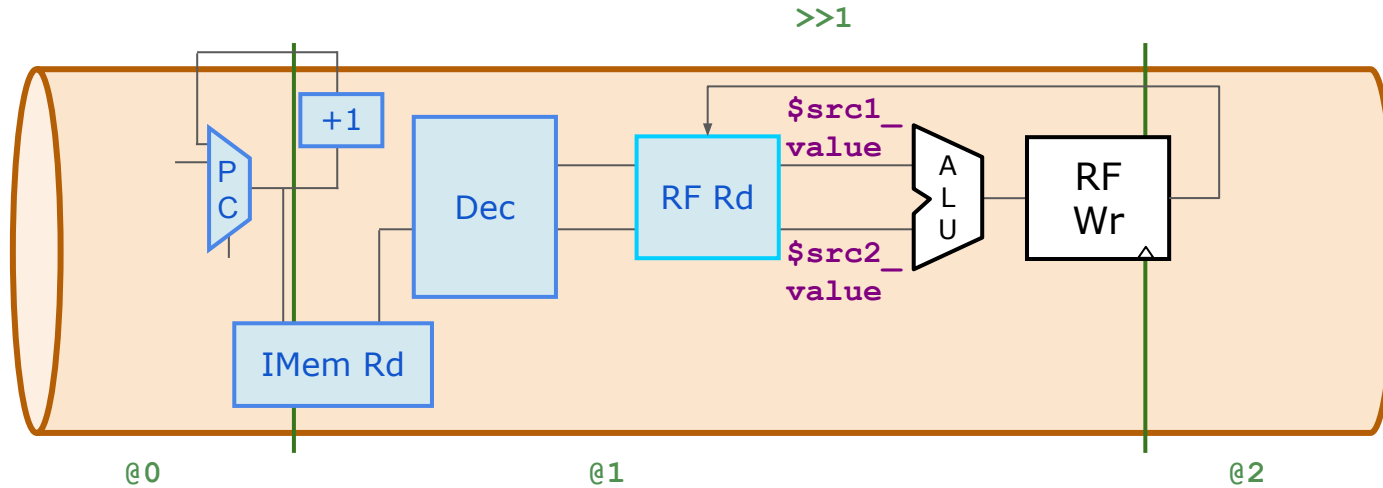

Assign `$src1/2_value[31:0]` to register file outputs.


Lab: ALU

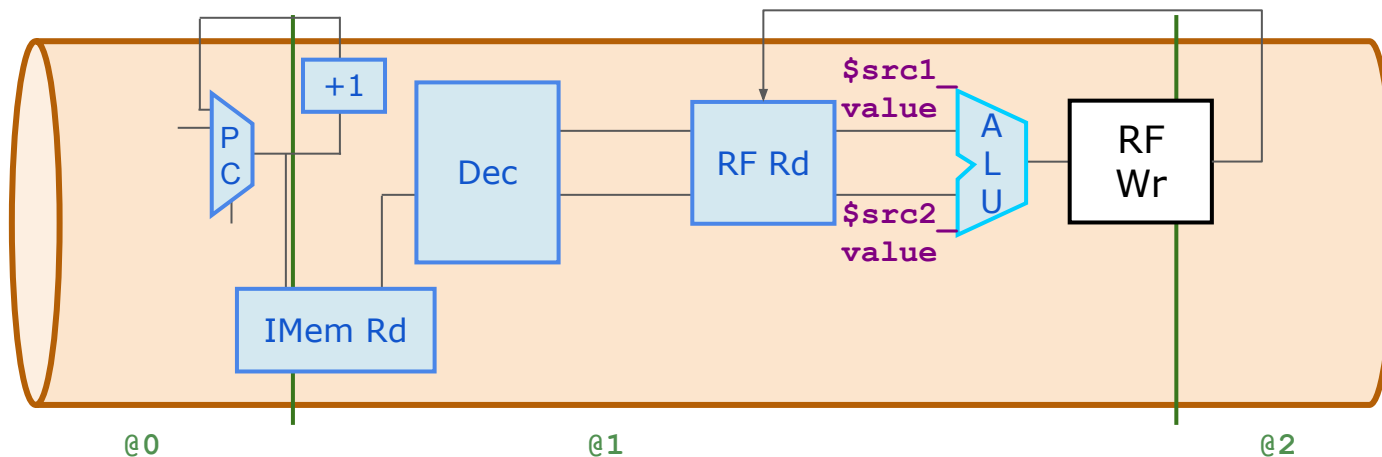Assign the ALU `$result` for ADD and ADDI. (You'll fill in others later.)



```
$result[31:0] =  
    $is_addi ? $src1_value + $imm :  
    ...  
    32'bx;
```


Register File Write

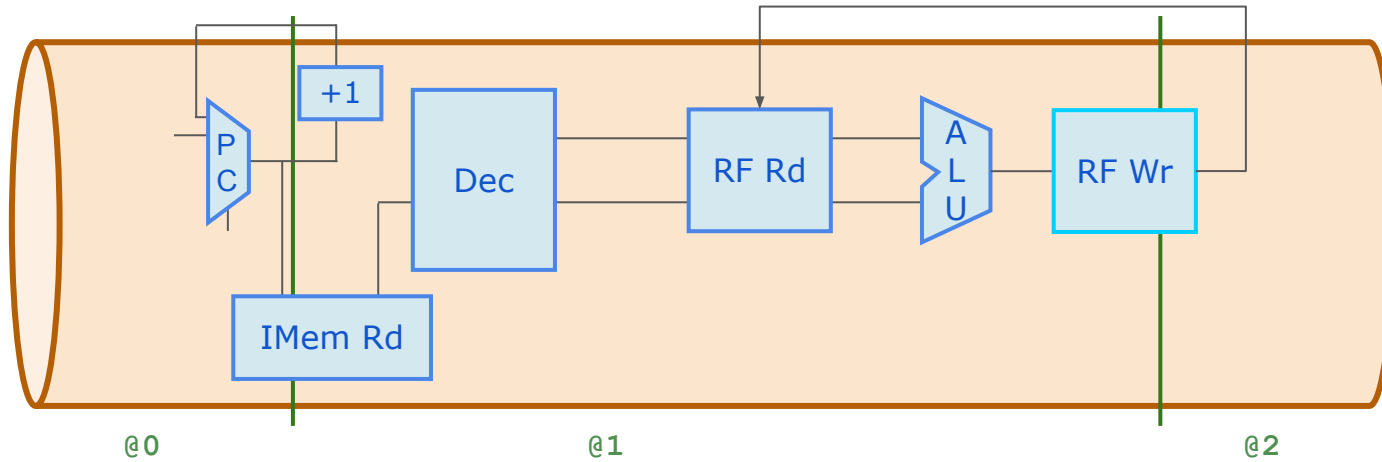

Lab: Register File Write


1. Provide proper input assignments to enable RF write (**wr**) of **\$result** to **\$rd** (dest reg) when **\$rd_valid** for a valid instruction.
2. Debug in simulation. Should be writing and reading registers.
3. But wait, in RISC-V, x0 is “always-zero”. Writes should be ignored. Add logic to disable write if **\$rd** is 0.
4. Save outside of Makerchip.

2-read, 1-write register file:

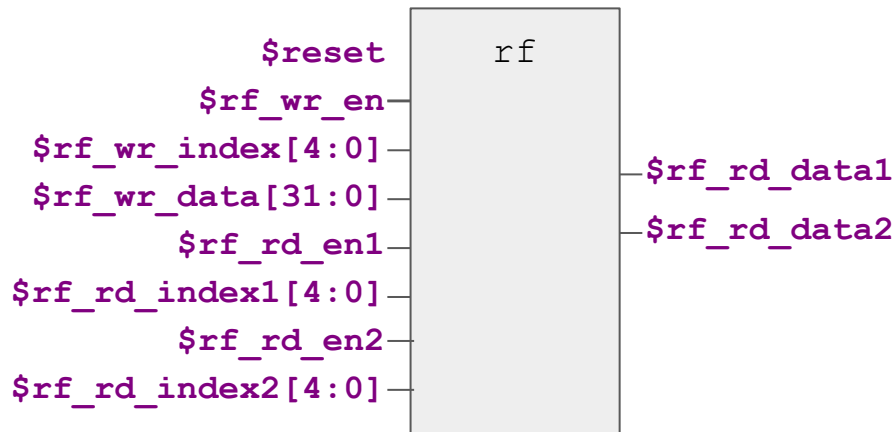


Arrays - What's inside?

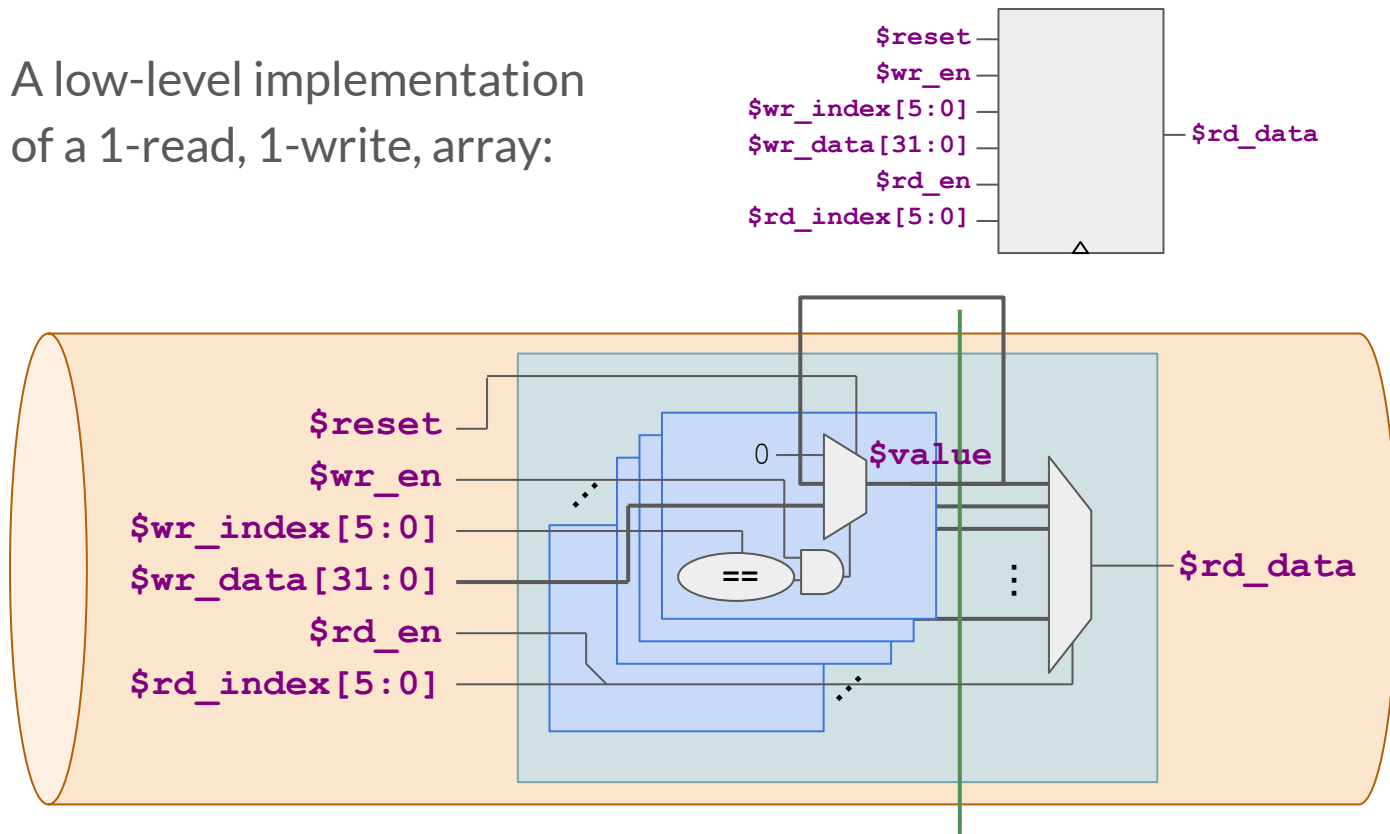
A low-level implementation
of a 1-read, 1-write, array:



Register File - Detailed

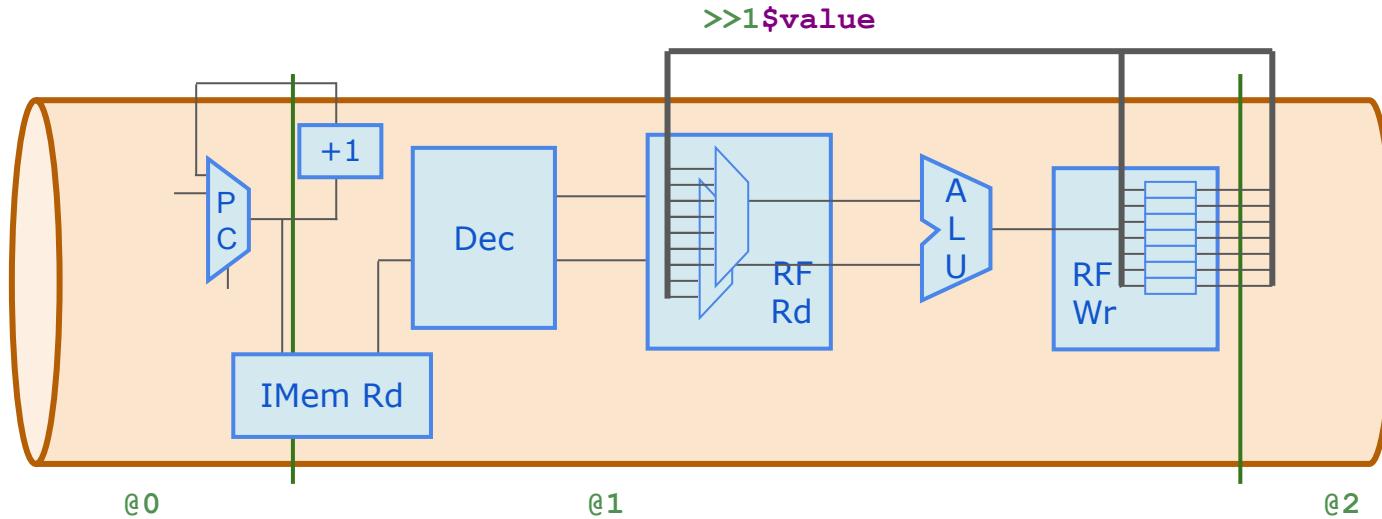


Lab: Branches

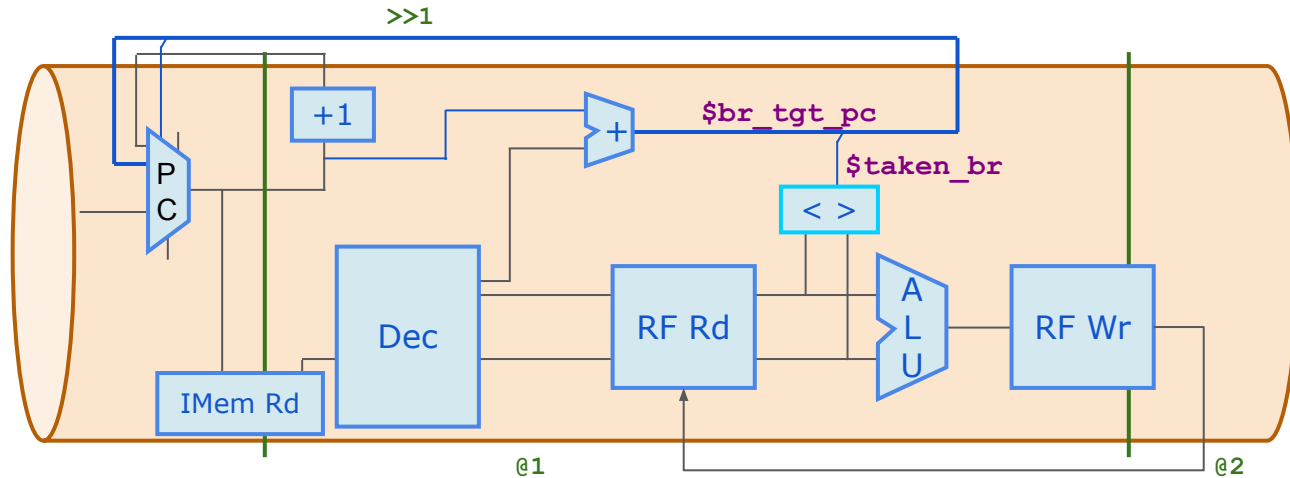

1. Determine **\$taken_br = ...** as a ternary expression based on **\$is_bxx**, defaulting to 1'b0.
2. Confirm save.

BEQ: ==
BNE: !=
BLT: (x1 < x2) ^ (x1[31] != x2[31])
BGE: (x1 >= x2) ^ (x1[31] != x2[31])
BLTU: <
BGEU: >=

Lab: Branches

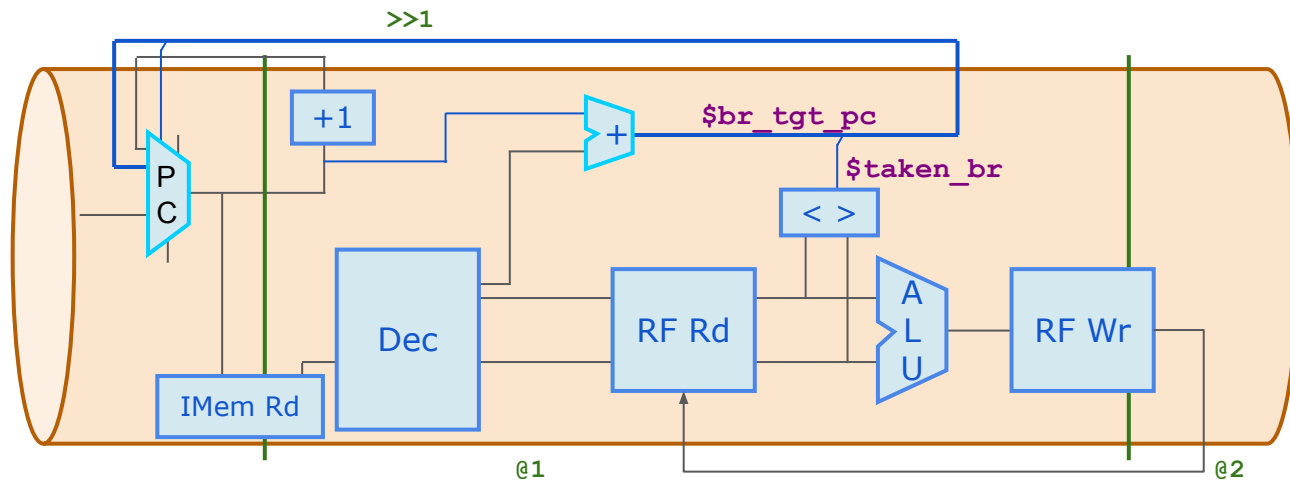

1. Compute $\$br_tgt_pc$ ($PC + imm$)
2. Modify $\$pc$ MUX expression to use the previous $\$br_tgt_pc$ if the previous instruction was $\$taken_br$.
3. Check behavior in simulation. Program should now sum values {1..9}!
4. Debug as needed, and save outside of Makerchip.


Lab: Testbench

Tell Makerchip when simulation passes by monitoring the value in register x10 (containing the sum) (within @1):


```
*passed = |cpu/xreg[10]>>5$value == (1+2+3+4+5+6+7+8+9) ;
```

Check log for passed message.


Pipelining Your RISC-V

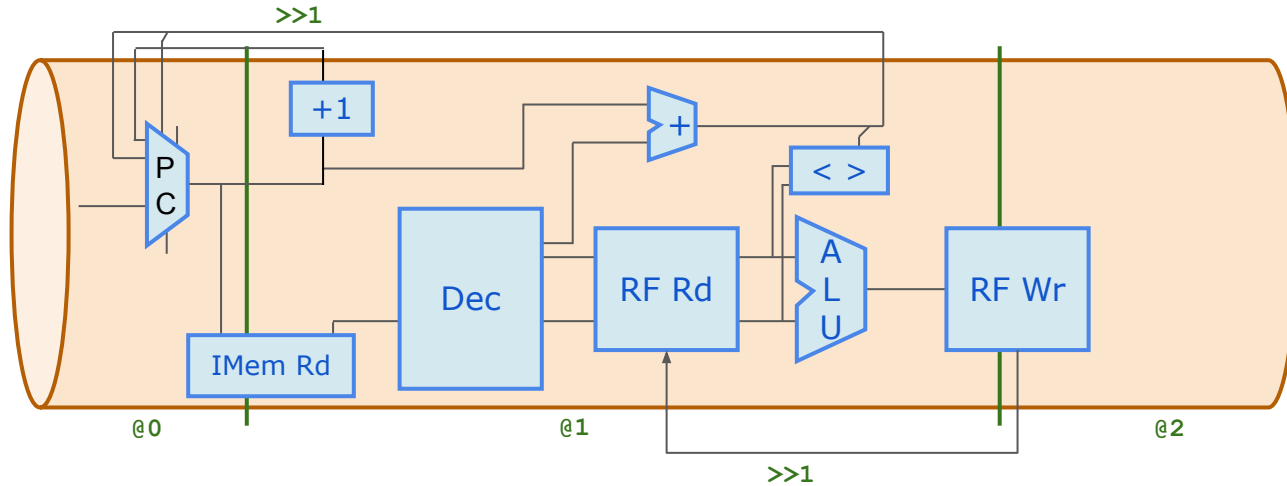


Waterfall Logic Diagram

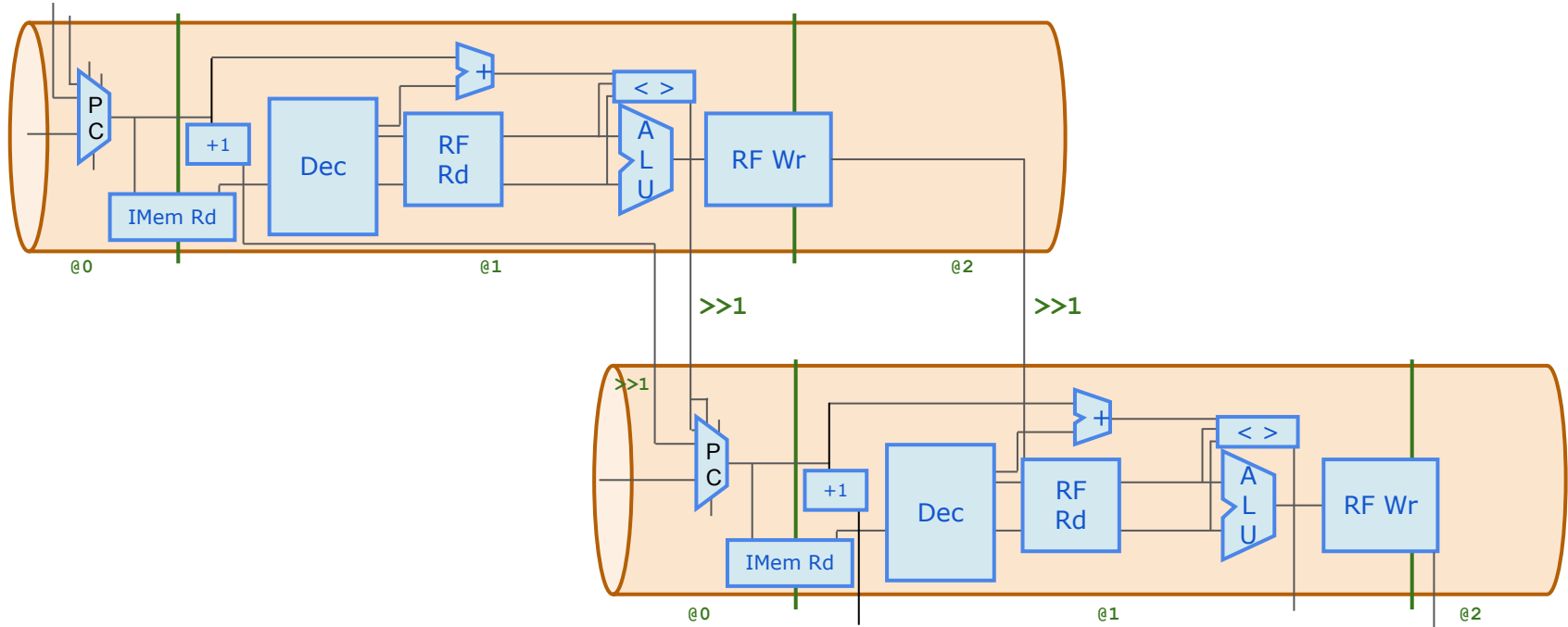


Pipelining Your RISC-V

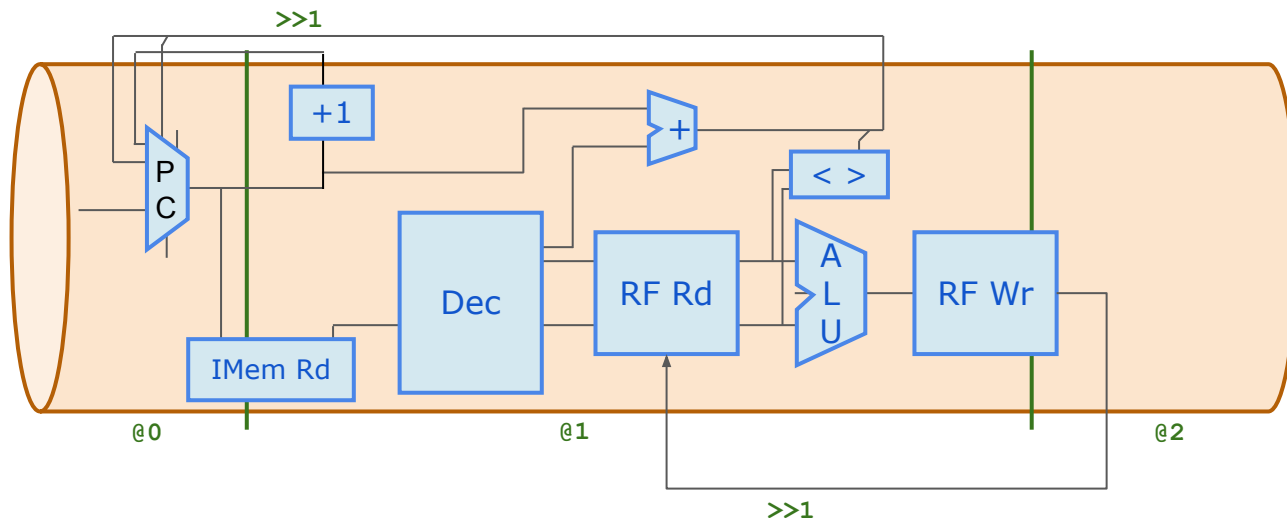


Pipelining Your RISC-V

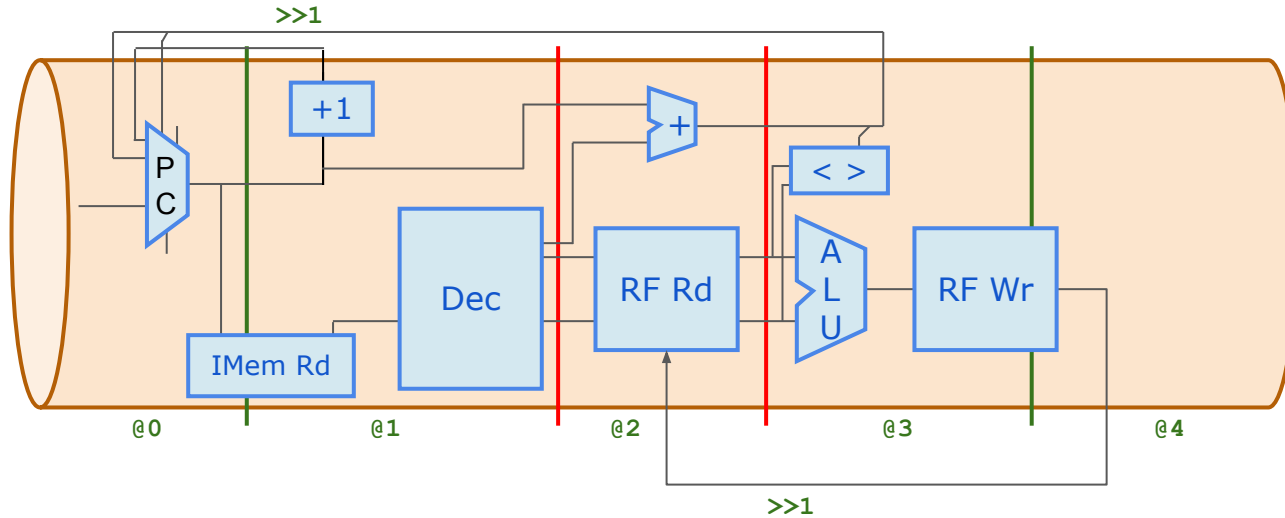


Waterfall Logic Diagram

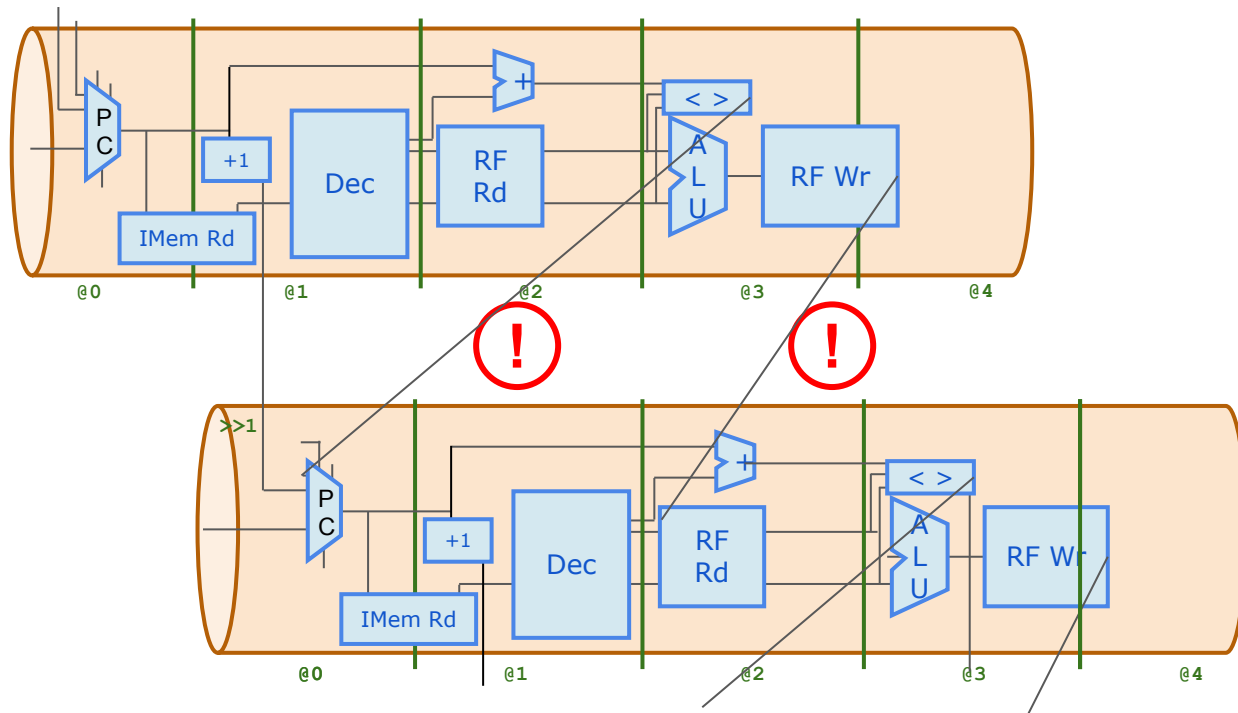


Pipelining Your RISC-V

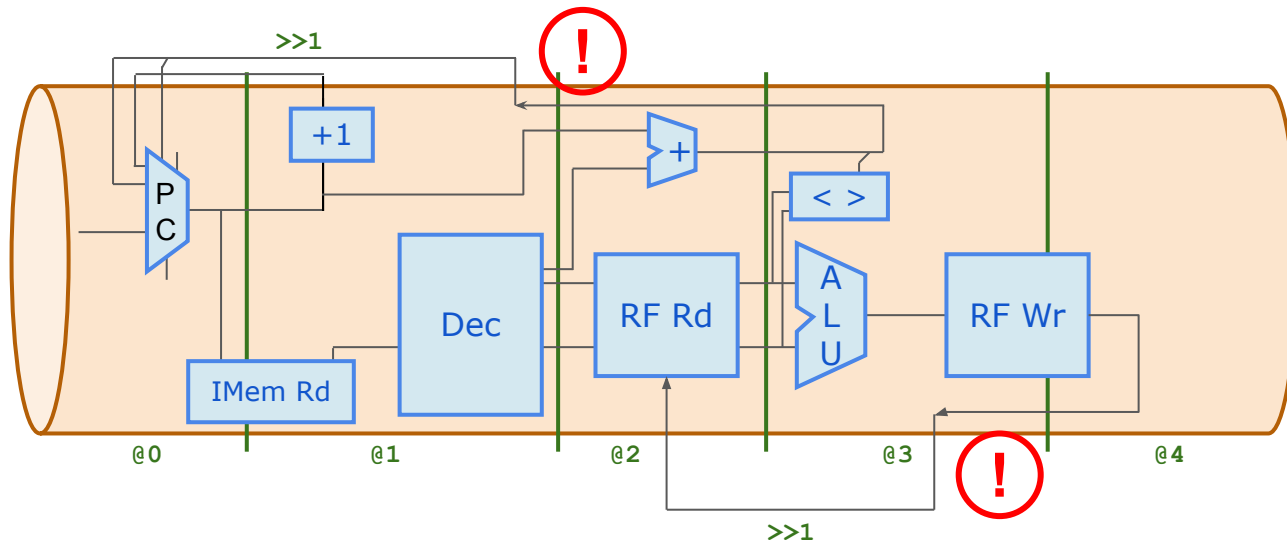


RISC-V Waterfall Diagram & Hazards

 


Time ->

 


RISC-V Waterfall Diagram & Hazards

 


Waterfall Logic Diagram

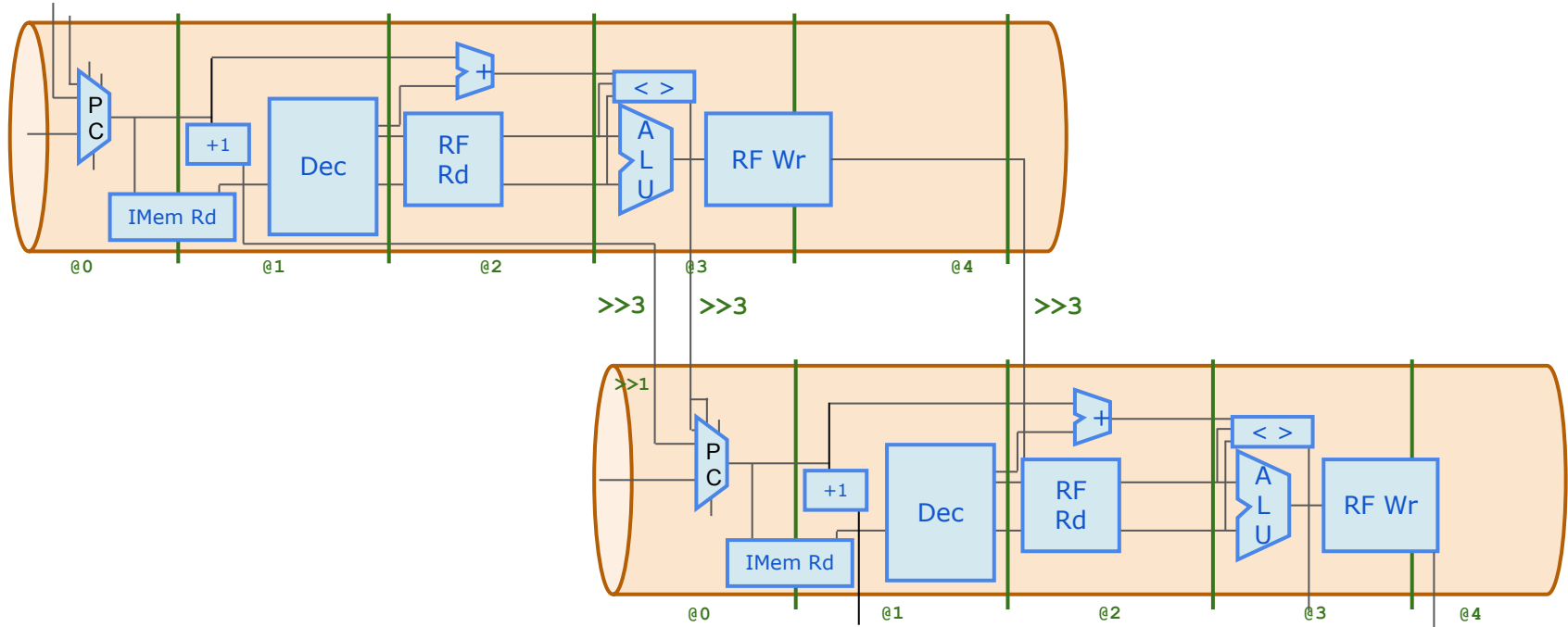


Lab: 3-Cycle \$valid

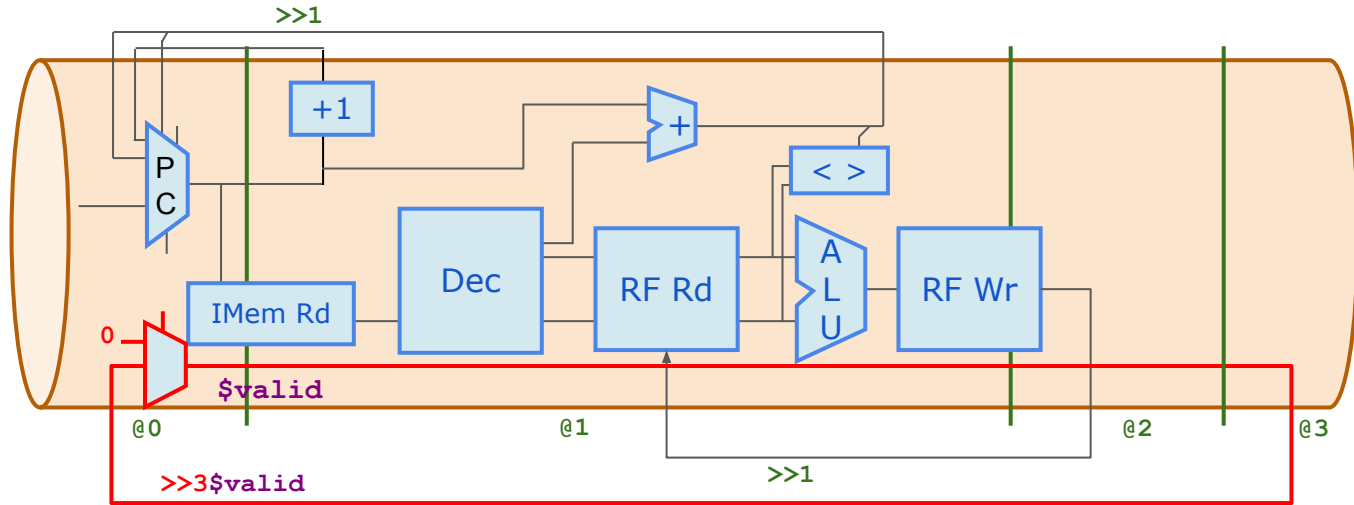

 1. Create `$start` to provide first `$valid` pulse (reset last cycle, but not this cycle).
2. Create `$valid: 0` during `$reset`, 1 for `$start`, `>>3$valid` o/w. Check simulation.




Lab: 3-Cycle RISC-V

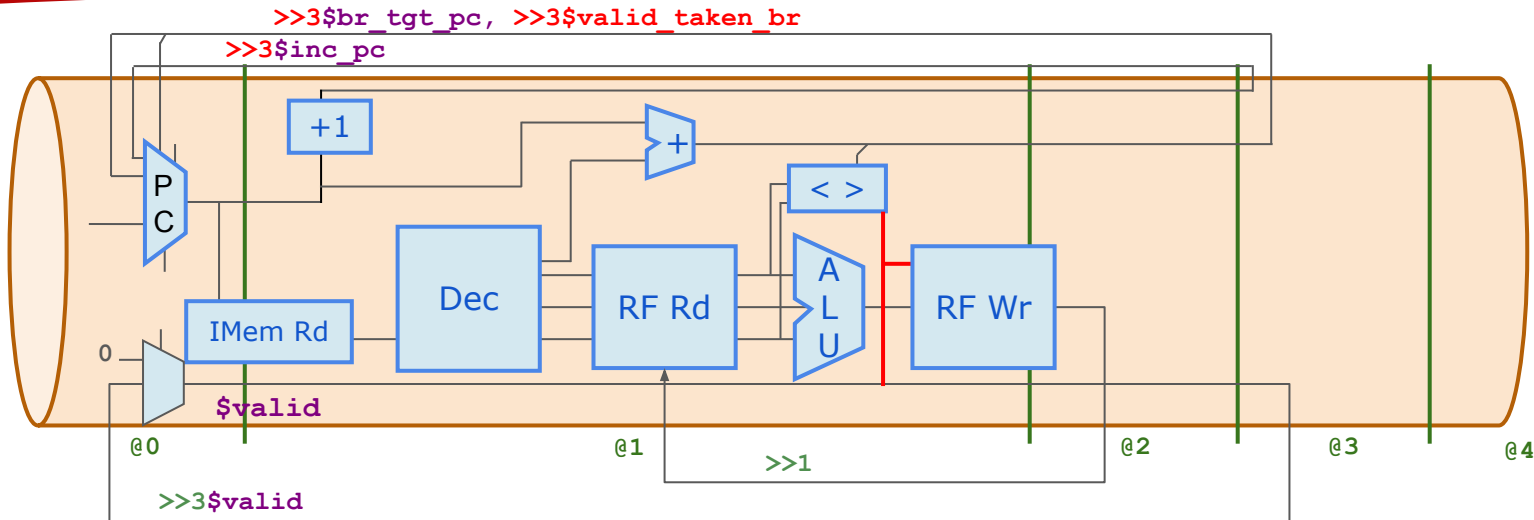

1. Avoid writing RF for invalid instructions.
2. Avoid redirecting PC for invalid (branch) instructions.
Introduce: `$valid_taken_br = $valid && $taken_br`; and use it in PC mux.
3. Update inter-instruction dependency alignments (`>>3`).
4. Debug until passing. Confirm save.


Lab: 3-Cycle RISC-V

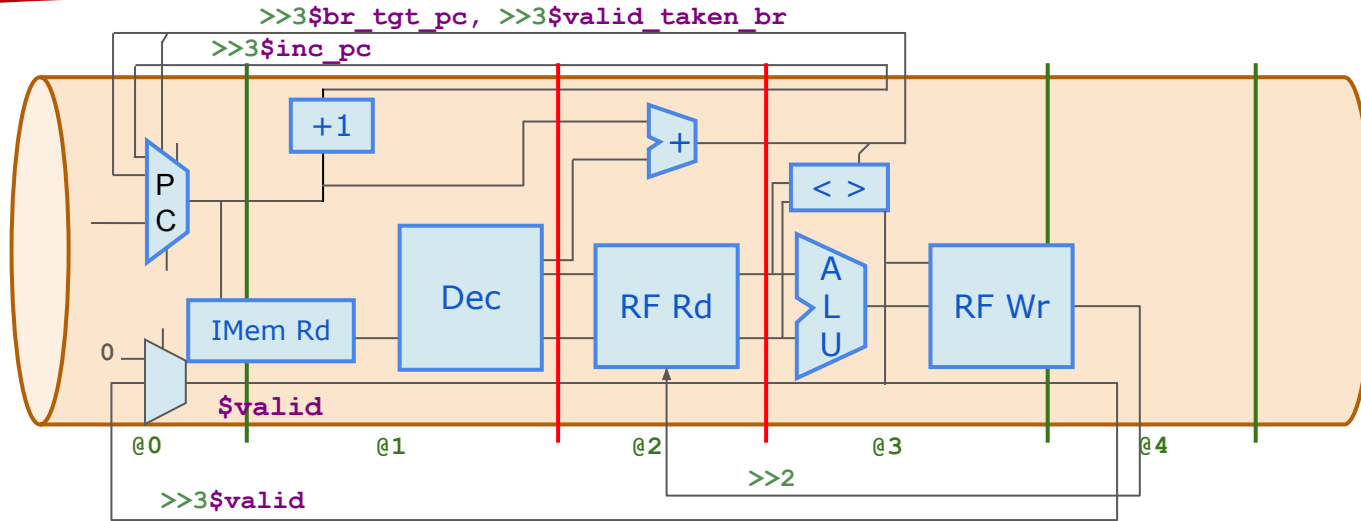


1. Partition logic into pipeline stages as above. Add stages; cut-n-paste code.
2. For RF use `m4+rf (@2, @3)`, implying `>>2`. (Since previous 2 instructions do not update RF, `>>1`, `>>2`, `>>3` are functionally equivalent.)
3. Debug as needed.

(You just changed most of your RTL code and added many lines!)


~1 Instruction Per Cycle (~1 IPC)

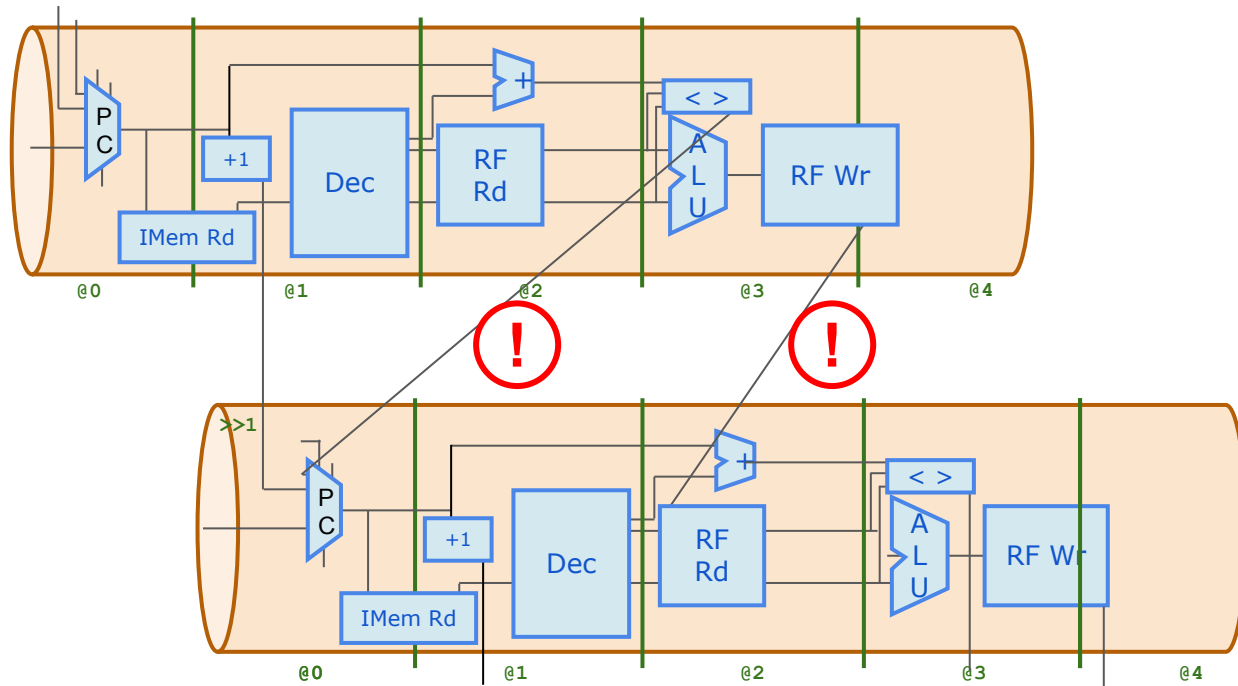

Register File Bypass

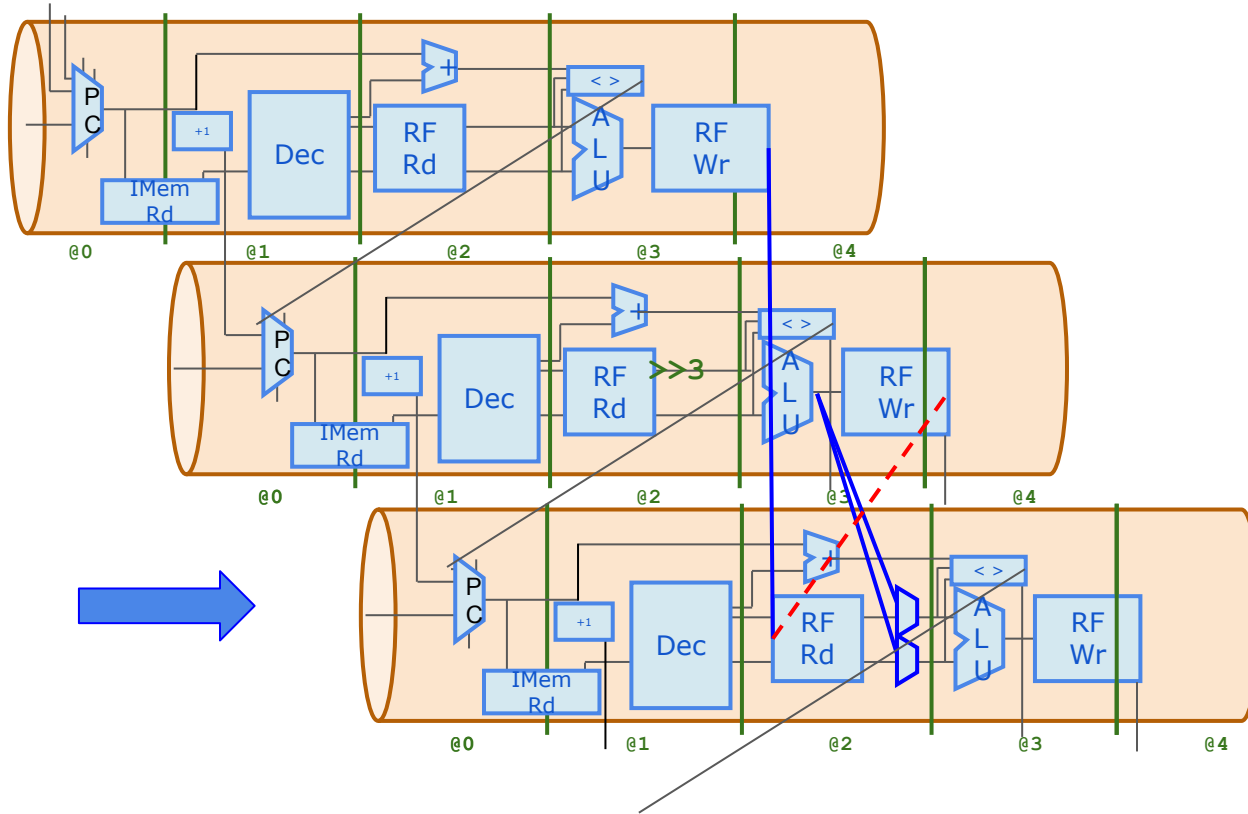


Lab: Register File Bypass

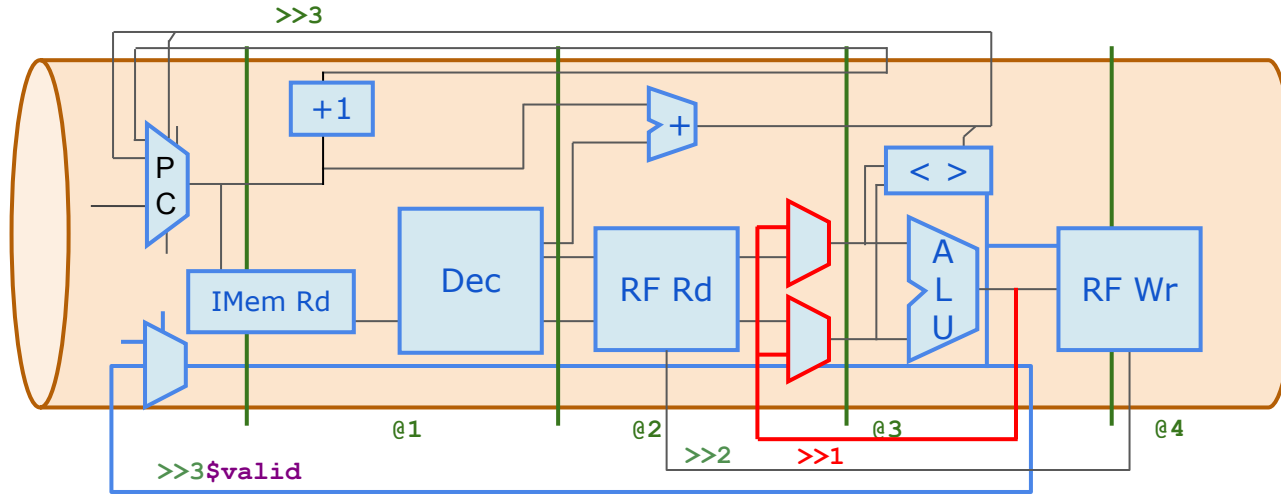


1. RF read uses RF as written 2 instructions ago (already correct).
2. Update expressions for $\$srcx_value$ to select previous $\$result$ if it was written to RF (write enable for RF) and if previous $\$rd == \rsx .
3. (Should have no effect yet)


Branches

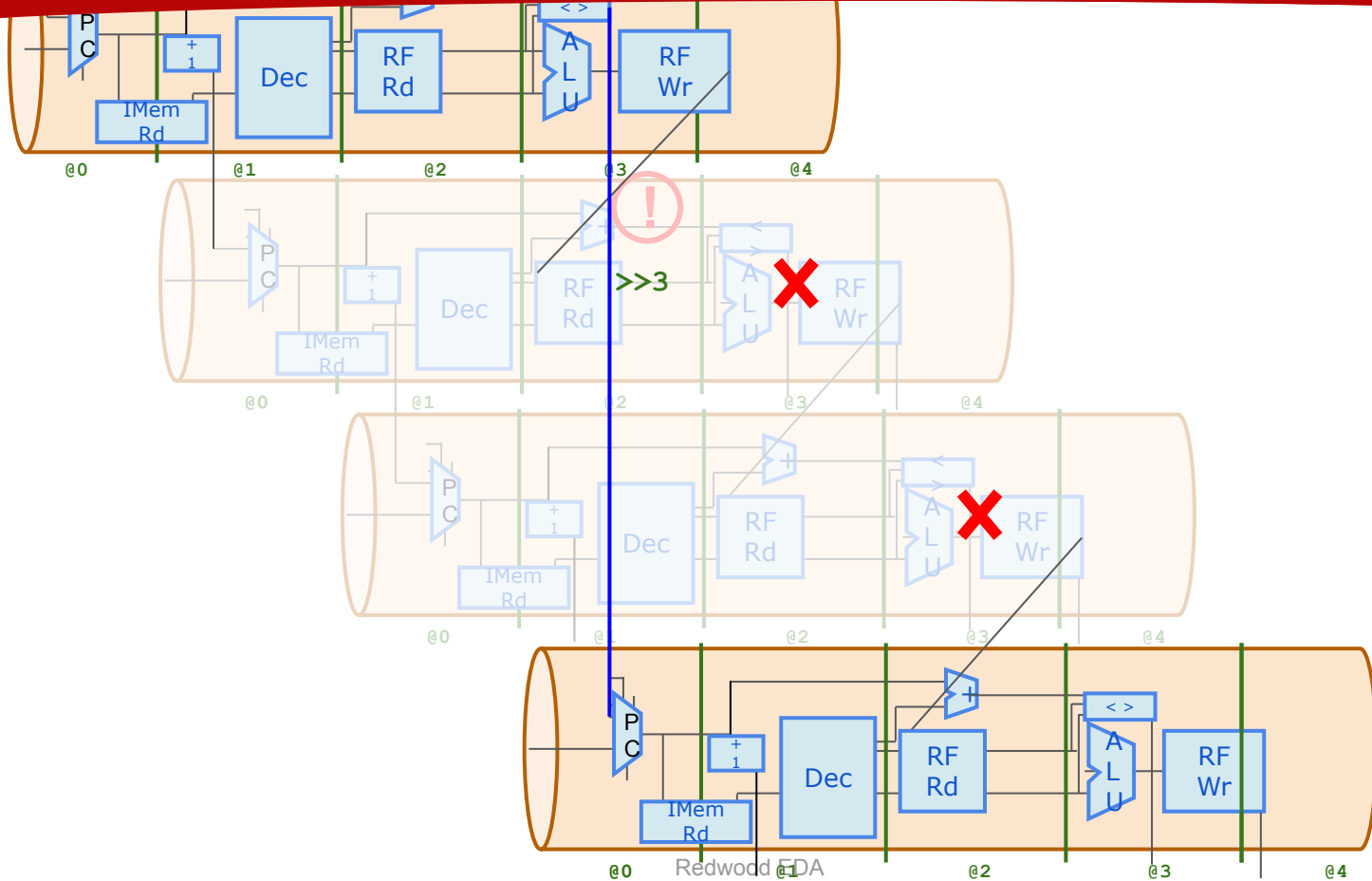


Branches

 

Time ->

 

Lab: Branches

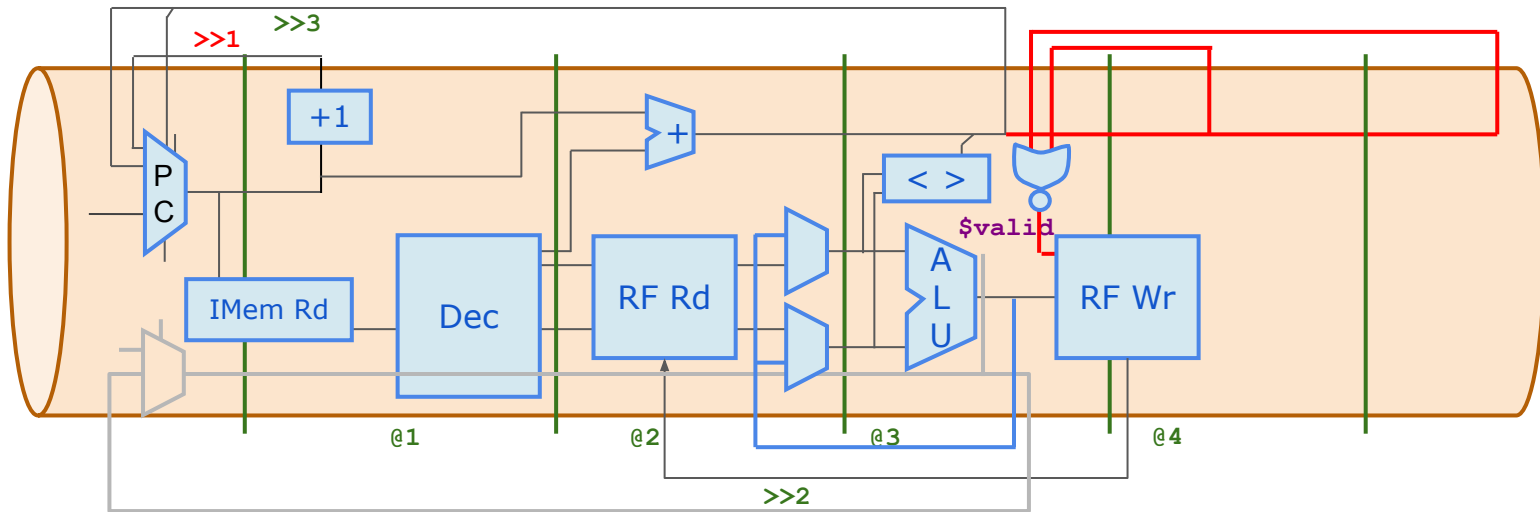

1. Replace @0 \$valid assignment with @3 \$valid assignment based on the non-existence of a valid \$taken_br's in previous two instructions.
2. Increment PC every cycle (not every 3 cycles)
3. (PC redirect for branches is already 3-cycle. No change.)
4. Debug. Save outside of Makerchip.

Lab: Complete Instruction Decode

RV32I Base Instruction Set (except FENCE, ECALL, EBREAK):

opcode		
	01101111	LUI
	00101111	AUIPC
	11011111	JAL
	11001111	JALR
000	1100011	BEQ
001	1100011	BNE
100	1100011	BLT
101	1100011	BGE
110	1100011	BLTU
111	1100011	BGEU
000	0000011	LB
001	0000011	LH
010	0000011	LW
100	0000011	LBU
101	0000011	LHU
000	0100011	SB
001	0100011	SH
010	0100011	SW
000	0010011	ADDI
010	0010011	SLTI

func7[5]	func3	opcode	
0	011	0010011	SLTIU
0	100	0010011	XORI
0	110	0010011	ORI
0	111	0010011	ANDI
0	001	0010011	SLLI
0	101	0010011	SRLI
0	101	0010011	SRAI
0	000	0110011	ADD
1	000	0110011	SUB
0	001	0110011	SLL
0	010	0110011	SLT
0	011	0110011	SLTU
0	100	0110011	XOR
0	101	0110011	SRL
1	101	0110011	SRA
0	110	0110011	OR
0	111	0110011	AND

1. Complete remaining instrs, except loads (L*).

```
$dec_bits[10:0] =  
    {$func7[5], $func3, $opcode};  
$is_beq = $dec_bits ==?  
    11'bx_000_1100011;
```

```
// Until instrs are implemented,  
// quiet down the warnings.  
'BOGUS_USE($is_beq $is_bne ...)
```

2. We'll treat all loads the same, so generate `$is_load` based on opcode only.
3. Confirm save.

Lab: Complete ALU


Assign **\$result** for other instrs

```
ANDI  $src1_value & $imm;  
ORI   $src1_value | $imm;  
XORI  $src1_value ^ $imm;  
ADDI  $src1_value + $imm;  
SLLI  $src1_value << $imm[5:0];  
SRLI  $src1_value >> $imm[5:0];  
AND    $src1_value & $src2_value;  
OR     $src1_value | $src2_value;  
XOR    $src1_value ^ $src2_value;  
  
SRAI  { {32{$src1_value[31]}}, $src1_value } >> $imm[4:0];  
SLT    ($src1_value[31] == $src2_value[31]) ? $slt_rslt : {31'b0, $src1_value[31]};  
SLTI   ($src1_value[31] == $imm[31]) ? $sltiu_rslt : {31'b0, $src1_value[31]};  
SRA    { {32{$src1_value[31]}}, $src1_value } >> $src2_value[4:0];
```

```
ADD    $src1_value + $src2_value;  
SUB    $src1_value - $src2_value;  
SLL    $src1_value << $src2_value[4:0];  
SRL    $src1_value >> $src2_value[4:0];  
SLTU   $src1_value < $src2_value;  
SLTIU  $src1_value < $imm;  
LUI    { $imm[31:12], 12'b0 };  
AUIPC  $pc + $imm;  
JAL     $pc + 4;  
JALR    $pc + 4;
```

Need intermediate
result signals for these.

Loads/Stores

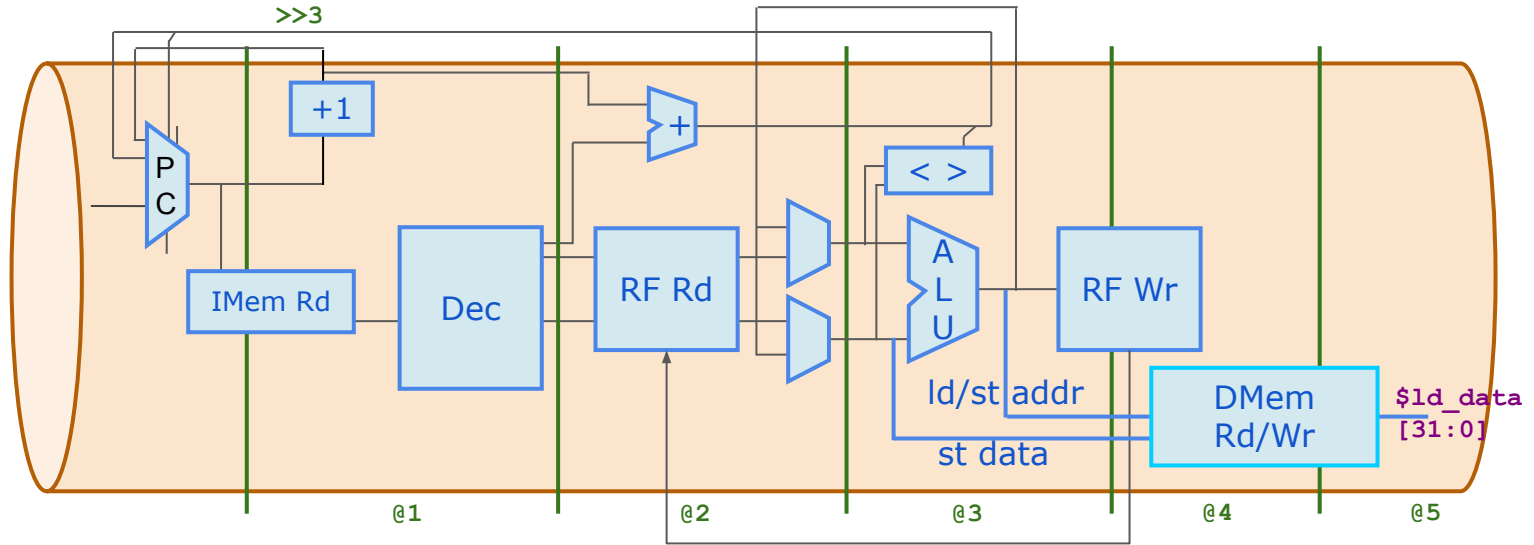

LOAD (LW, LH, LB, LHU, LBU)

LOAD rd, imm(rs1)

rd <= DMem[addr]


STORE (SW, SH, SB)

STORE rs2, imm(rs1)


DMem[addr] <= rs2

where, addr <= rs1 + imm (like addi)


Loads

 


Time ->

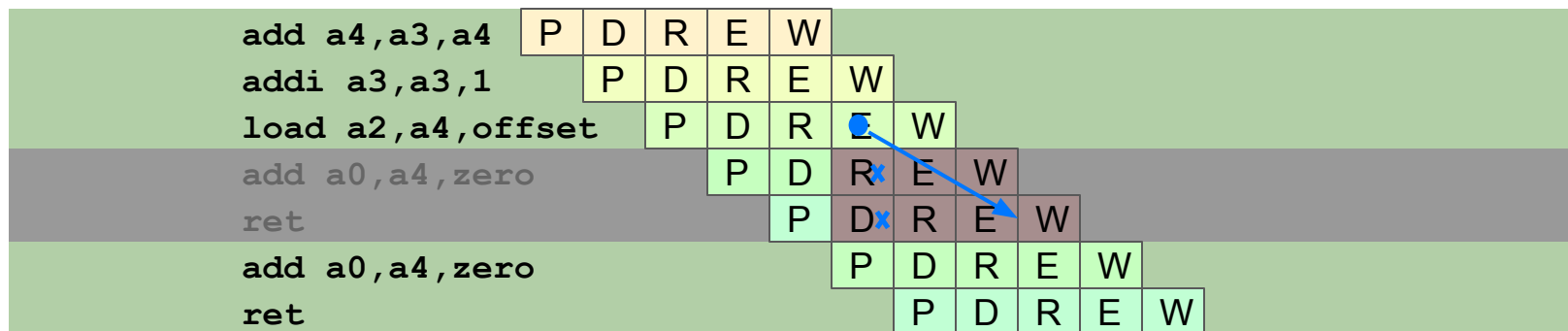

Loads

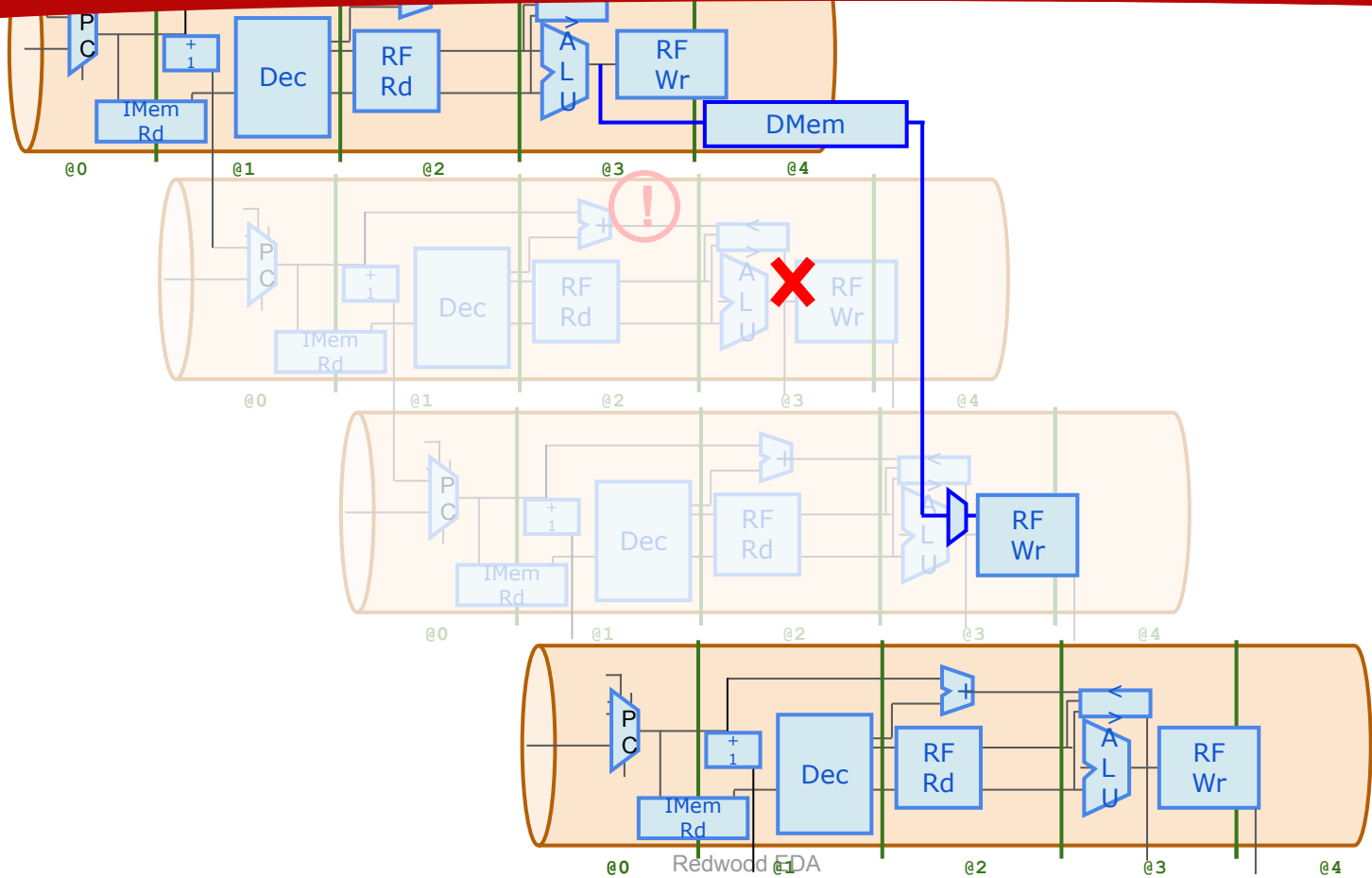


Lab: Redirect Loads

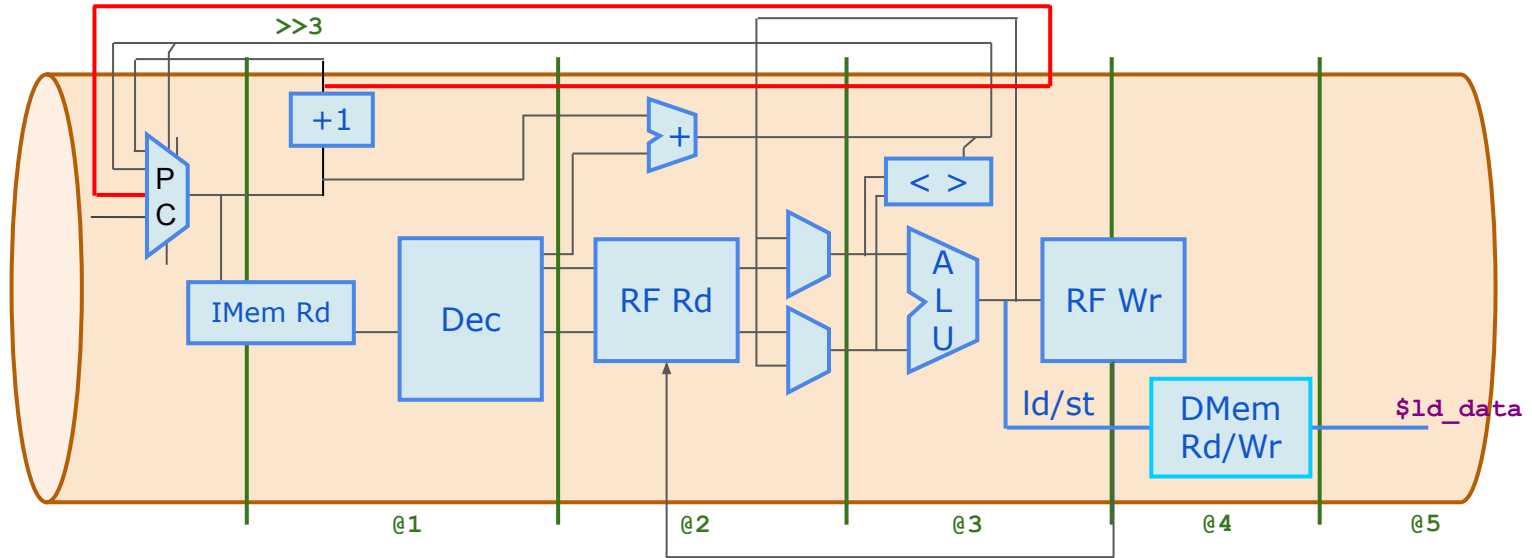

1. Clear **\$valid** in the “shadow” of a load (like branch).
2. Select **\$inc_pc** from 3 instructions ago for load redirect.
3. Debug. Confirm save.


Lab: Load Data

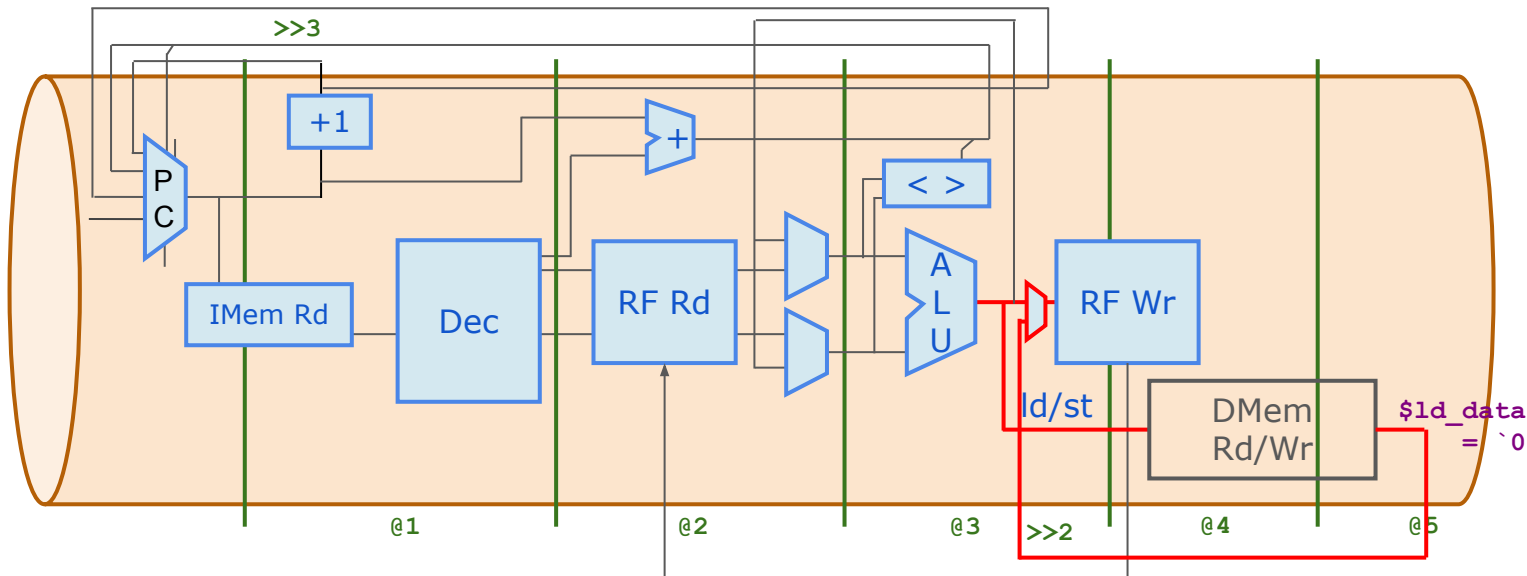


1. For loads/stores ($\$is_load/\is_s_instr), compute same result as for `addi`.
2. Add the RF-wr-data MUX to select $\gg 2\$ld_data$ and $\gg 2\$rd$ as RF inputs for !
 $\$valid$ instructions.
3. Enable write of $\$ld_data$ 2 instructions after valid $\$load$.
4. Confirm save.

Also provide the right register index for the write of $\$ld_data$.

Lab: Load Data

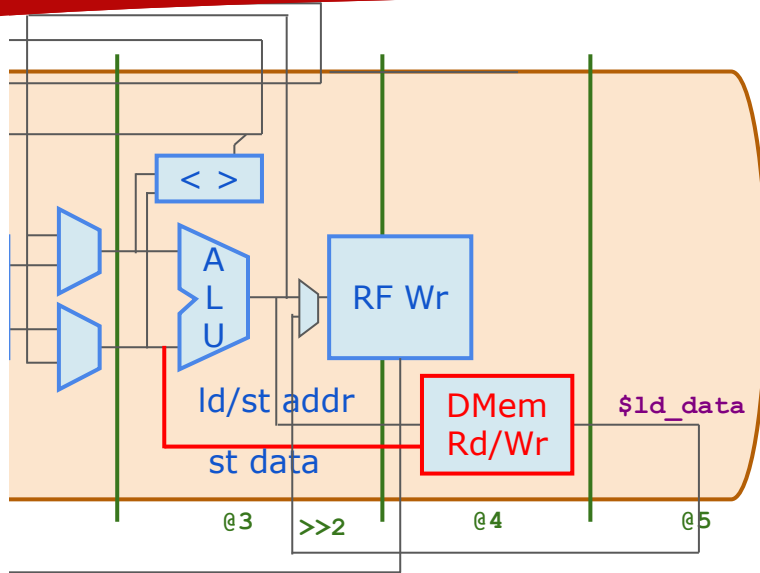

 dmem: mini 1-R/W memory
(16-entries, 32-bits wide)



1. Uncomment `//m4+dmem (@4)`.
2. Connect interface signals above using address bits [5:2] to perform load and store (when valid).



Lab: Load/Store in Program

Modify the test program to store the final result value to address 4, then load it into x15.


```
m4_asm(SW, r0, r10, 100)
```

```
m4_asm(LW, r15, r0, 100)
```

Update passing condition to look in `xreg[15]`.

Debug. Does the loop properly fall-through and execute store/load.


Jumps

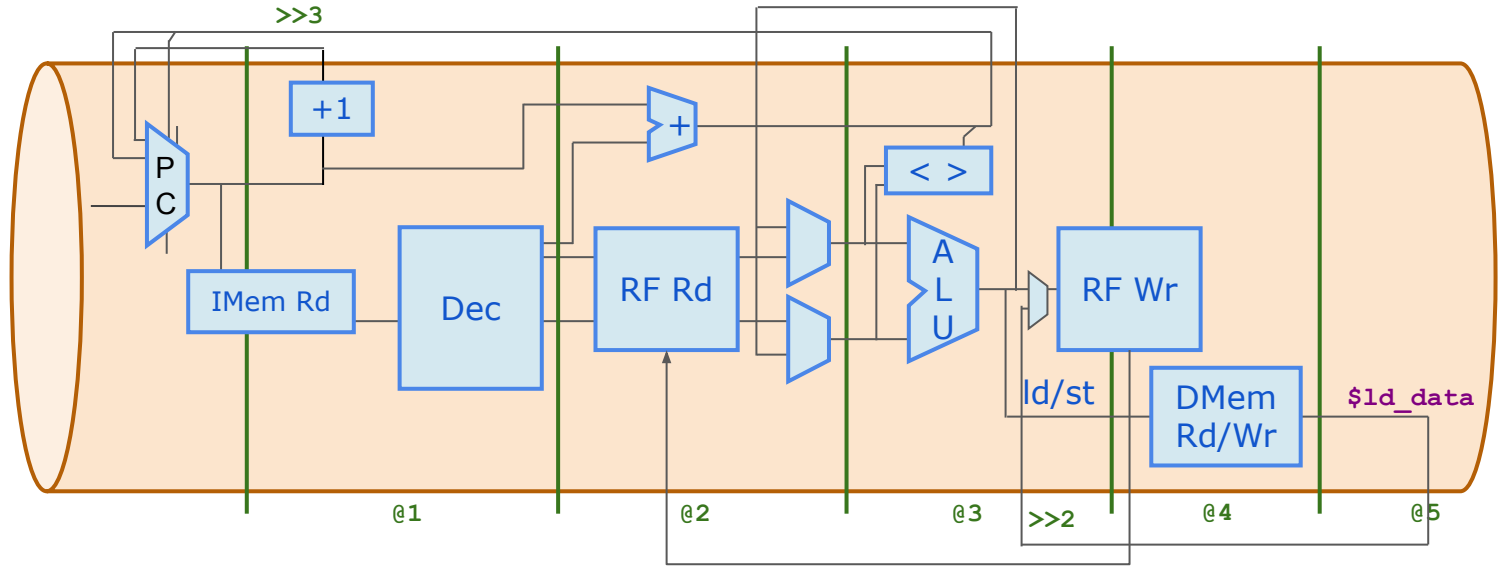

JAL: Jump to PC + IMM (aka unconditional branch, so $\$br_tgt_pc$)

JALR: Jumps to SRC1 + IMM.

Lab: Jumps

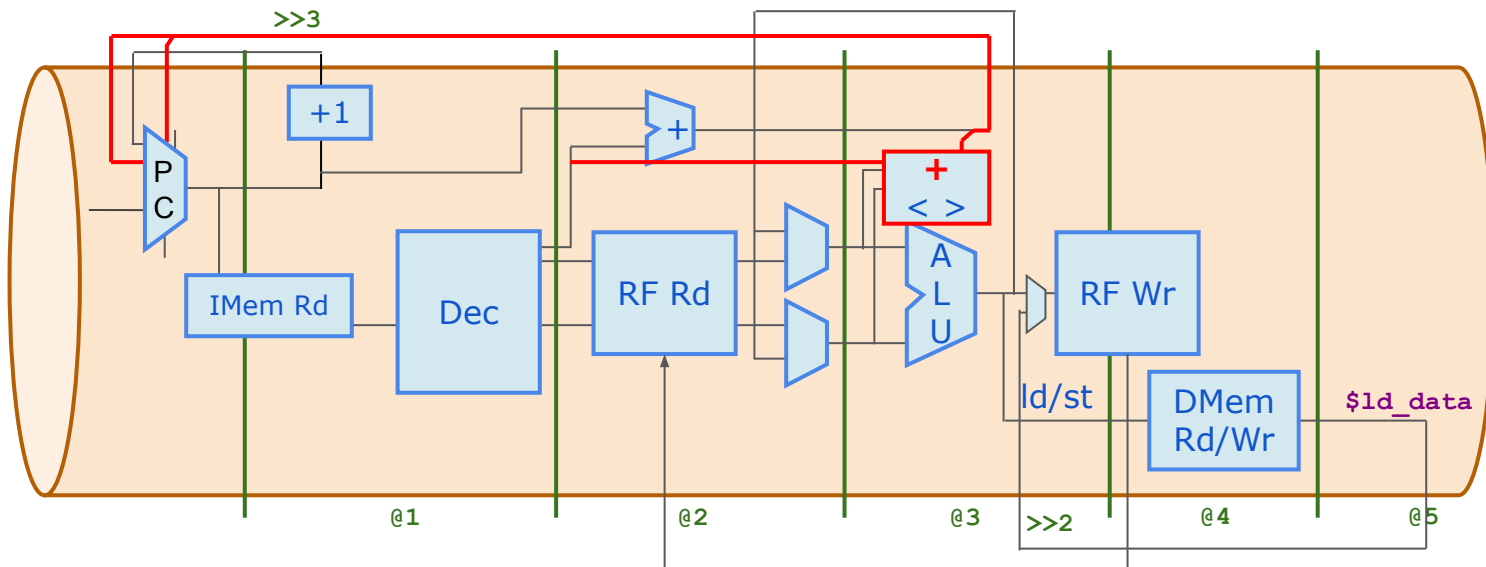

1. Define $\$is_jump$ (JAL or JALR), and, like $\$taken_br$, create invalid cycles.
2. Compute $\$jalr_tgt_pc$ (SRC1 + IMM).
3. Select correct $\$pc$ for JAL ($\gg 3 \$br_tgt_pc$) and JALR ($\gg 3 \$jalr_tgt_pc$).
4. Save.



YOU DID IT!!!!!!

Skills You Have Acquired

- Digital logic design
- CPU microarchitecture
- Knowledge of RISC-V ISA
- TL-Verilog
- Makerchip

Funda-
mental
Skills!

Crazy-
Hot
Topic!

Latest
Technology!



Next Steps

- Explore other resources available in Makerchip.
 - Learn more TL-Verilog. Tutorials, etc. for hierarchy, state, transactions
 - Learn Visual Debug
 - Learn M5 macro preprocessing
- Capture your work in GitHub.
- Share your experience on social media.
- Join community forums and follow social media feeds.